

# **Designing Stability into 1296 MHz and 2304 MHz Low Noise Amplifiers**

**By Al Ward W5LUA & Tommy Henderson WD5AGO**

**July 28, 2007**

**Central States VHF Society**

**San Antonio, Texas**

## What do we want from an LNA?

**Low noise figure < 0.4 dB**

**High gain > 35 dB**

**Good input and output match – minimizes interactions with other stages**

**Stable – must not oscillate when connected to antenna**

**Cascadable**

## What makes a good second stage?

**Low noise figure < 0.8 dB NF**

**Enough gain to make cascade about 30 to 35 dB**

**Good broadband match for first stage**

**Stable**

# Today's Transistors

**Today's transistors have very low noise figures and very high gain**

**High gain contributes to stability problems and decreased input intercept point**

**Minimum input VSWR and minimum noise figure will generally not occur simultaneously with same matching network. Use of source inductance may help but too much may cause instability**



## ATF-3XXXX Series of PHEMTs

Depletion mode PHEMT technology – requires negative voltage on gate wrt source

Ceramic and plastic surface mount packaging

Various gate widths 200u / 400u / 800u / 1600 u

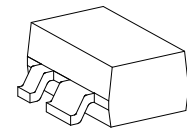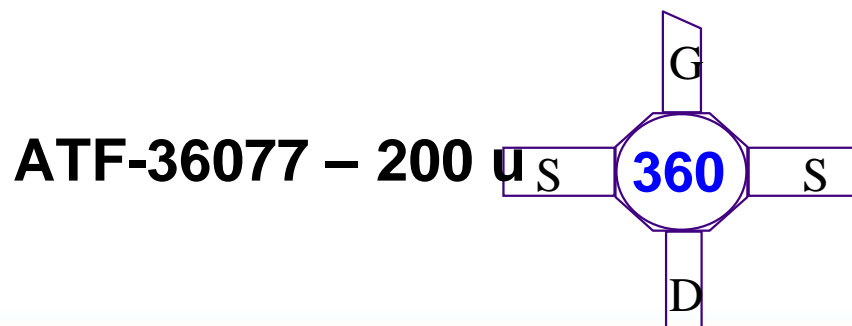At lower frequencies, i.e. 2 GHz or less, larger gate widths offer lower gain and lower impedances which can contribute to improved stability and lower matching circuit losses



ATF-35143 – 400 u  
ATF-34143 – 800 u  
ATF-33143 – 1600 u


## ATF-5XXX Series of PHEMTs

Enhancement mode PHEMT technology – requires positive voltage on gate wrt source

Plastic surface mount packaging

Various gate widths 400u / 800u and larger

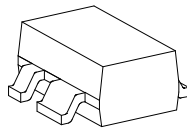Noise figure of enhancement mode devices 0.1 to 0.2 dB higher than depletion mode devices



**ATF-55143 – 400 u**

**ATF-54143 – 800 u**

# What about S-parameters?!??!


A three-terminal two-port, such as the FET shown, has four S-parameters.

$S_{nn}$  = voltage reflection coefficient, both amplitude and phase relative to  $50 \Omega$  source impedance

$S_{21}$  and  $S_{12}$  are commonly displayed on a polar chart.


$S_{11}$  =  $\Gamma_{\text{input}}$  displayed on Smith chart

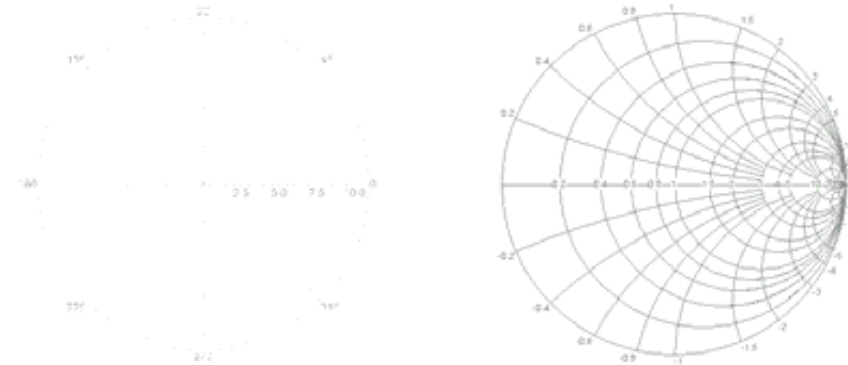$S_{22}$  =  $\Gamma_{\text{output}}$  displayed on Smith chart



Polar chart

Smith chart

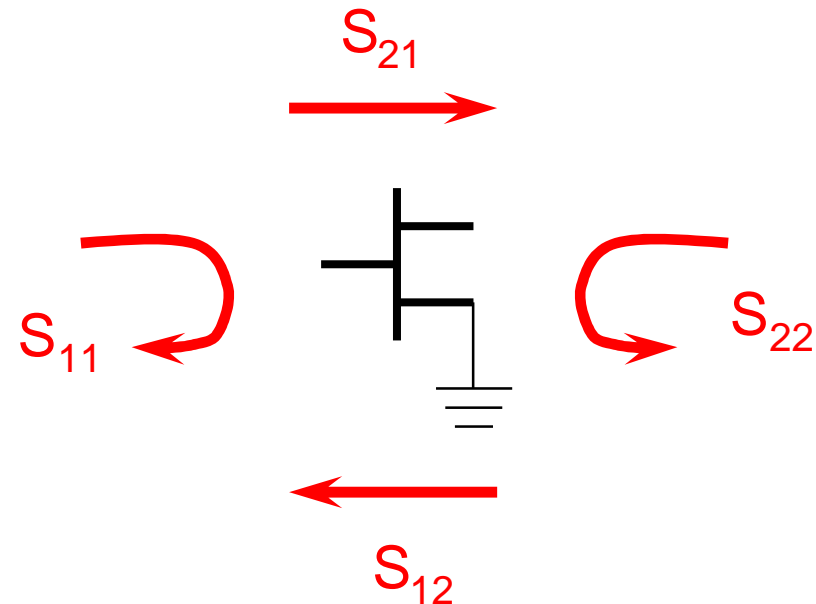


# What about Noise Parameters?!??!

$\Gamma_o$  (Gamma Opt) is the reflection coefficient of the source impedance presented to the device that allows the device to produce its'  $f_{min}$

Matching circuit losses often limit the ability of the amplifier to achieve a noise figure equivalent to device  $f_{min}$

$\Gamma_o$  not necessarily equal to  $S11^*$  which means noise match is not equivalent to a gain match

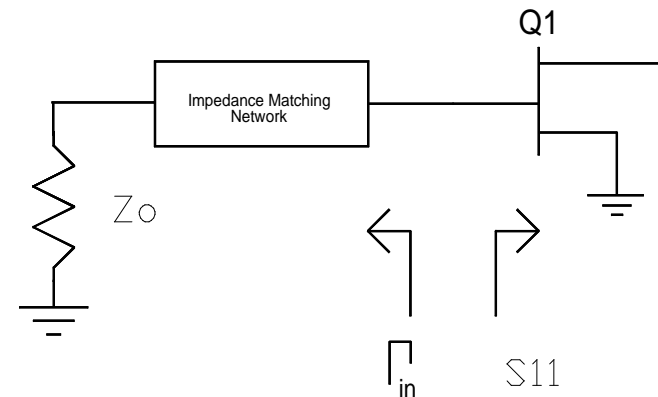$R_n$  (Noise Resistance) is used to calculate the device's sensitivity in noise figure to changes in source impedance,  $r_n$  is normalized to 50  $\Omega$ .



For minimum NF,  $\Gamma_{in} = \Gamma_o$   
 For maximum gain,  $\Gamma_{in} = S11^*$



## Other measures of input characteristics

**VSWR = Voltage Standing Wave Ratio**

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$



**Return Loss**

$$RL = 10 \log |\Gamma|^2$$

**Mismatch Loss**

$$ML = 10 \text{ LOG } (1 - \Gamma^2)$$

# Input Impedance Match

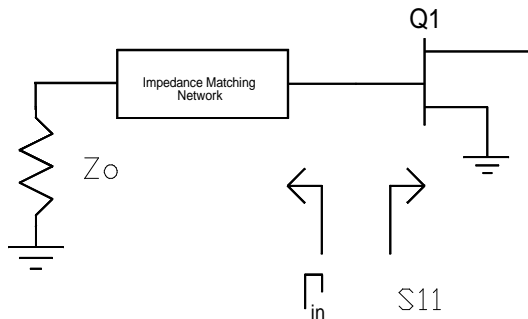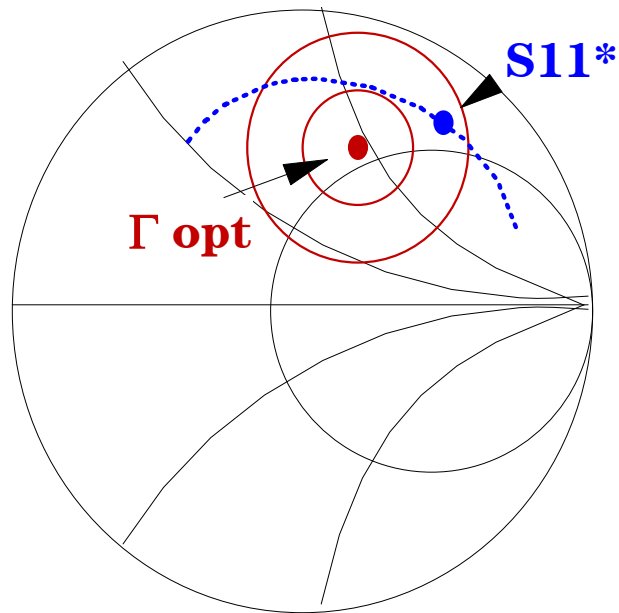


Match to  $\Gamma_{opt}$  for minimum noise figure

Noise degrades in circular contours as match moves away from  $\Gamma_{opt}$

Degree of noise degradation is dependent on  $R_n$ , the noise resistance

Most amateur applications aim for minimum noise figure and accept input VSWR
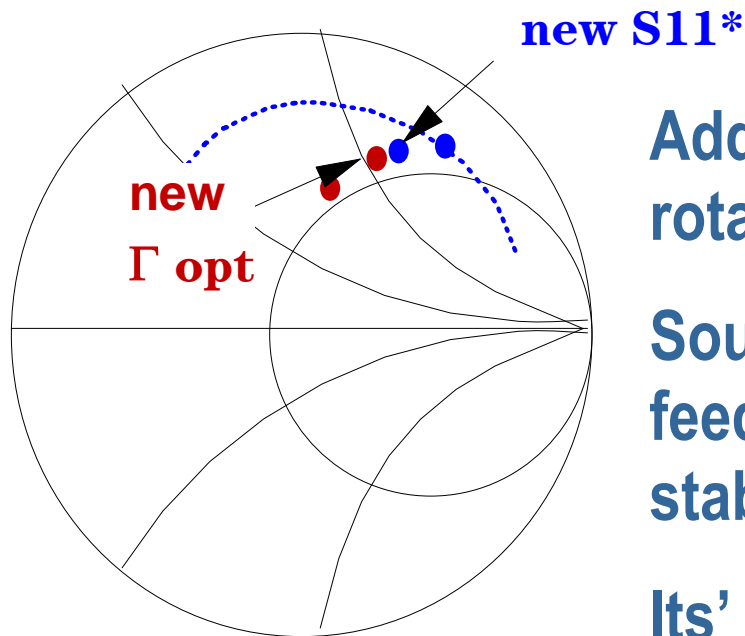
# Simultaneous Input VSWR and Noise Match




Adding source inductance rotates  $\Gamma_{opt}$  towards  $S_{11}^*$

Source inductance is series feedback which effects gain and stability

Its' effect must be analyzed over as a wide a bandwidth as the device has gain

## Output Impedance Match

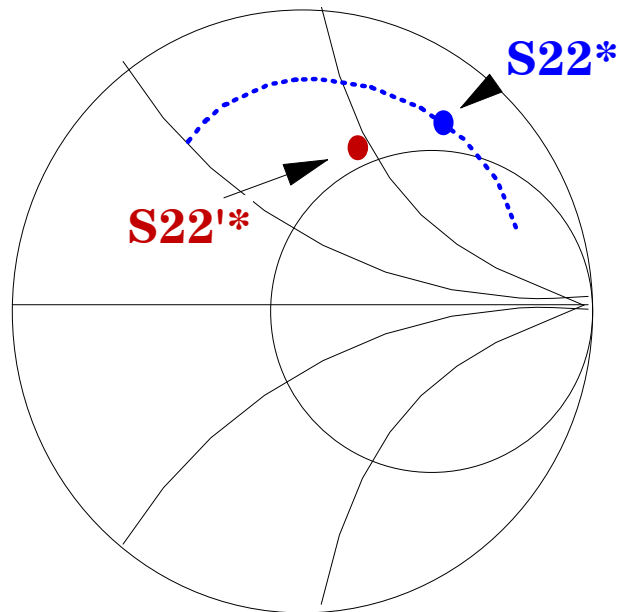

$$\Gamma_L = \left[ S_{22} + \frac{S_{12} S_{21} \Gamma_O}{1 - S_{11} \Gamma_O} \right]^*$$


$S_{22}'^* = \Gamma_L$  is the reflection coefficient of the output matching network with input terminated in  $\Gamma_{opt}$ , not  $50\Omega$

Match to  $S_{22}'^* = \Gamma_L$  for best gain/output VSWR

LNA may not be unconditionally stable when matched for best output VSWR - Some resistive loading may be required to reduce gain to improve stability

Best output VSWR does not necessarily guarantee best P1dB and IP3.


# Using AppCAD for Circuit Analysis

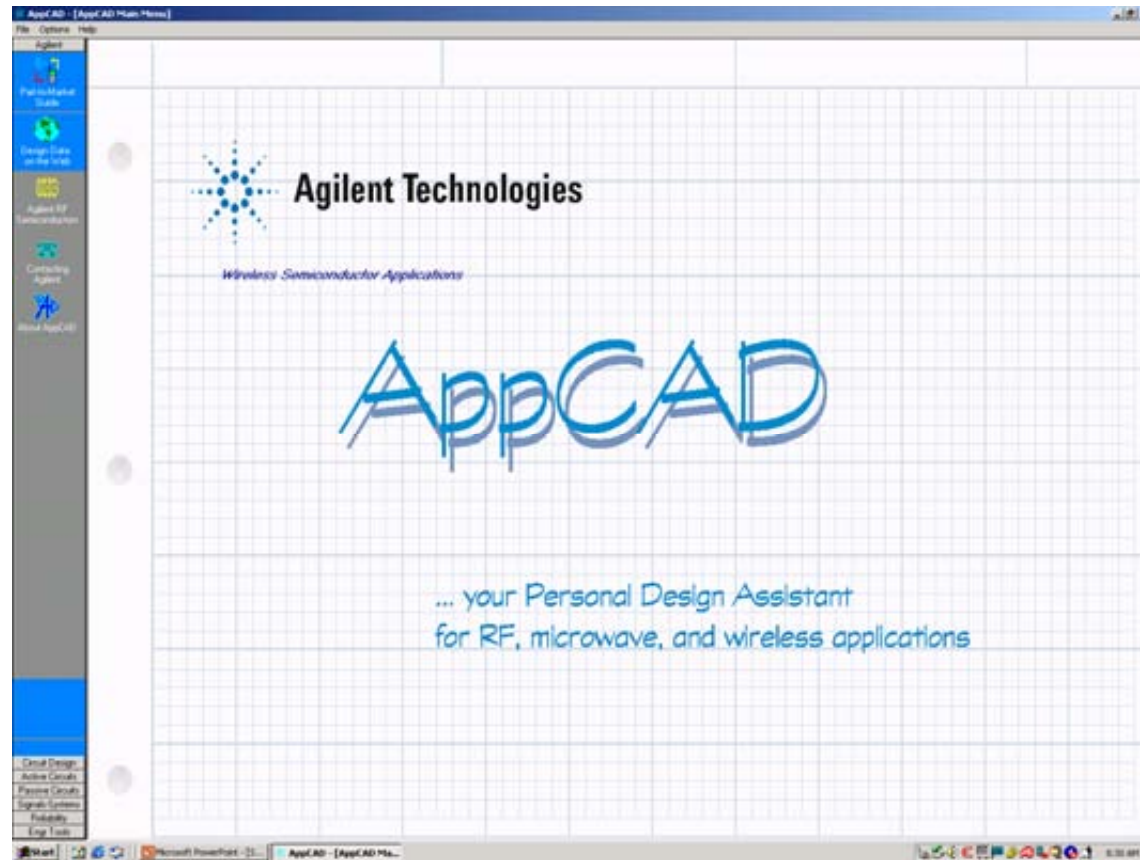

Available for free  
download at

<http://www.avagotech.com>
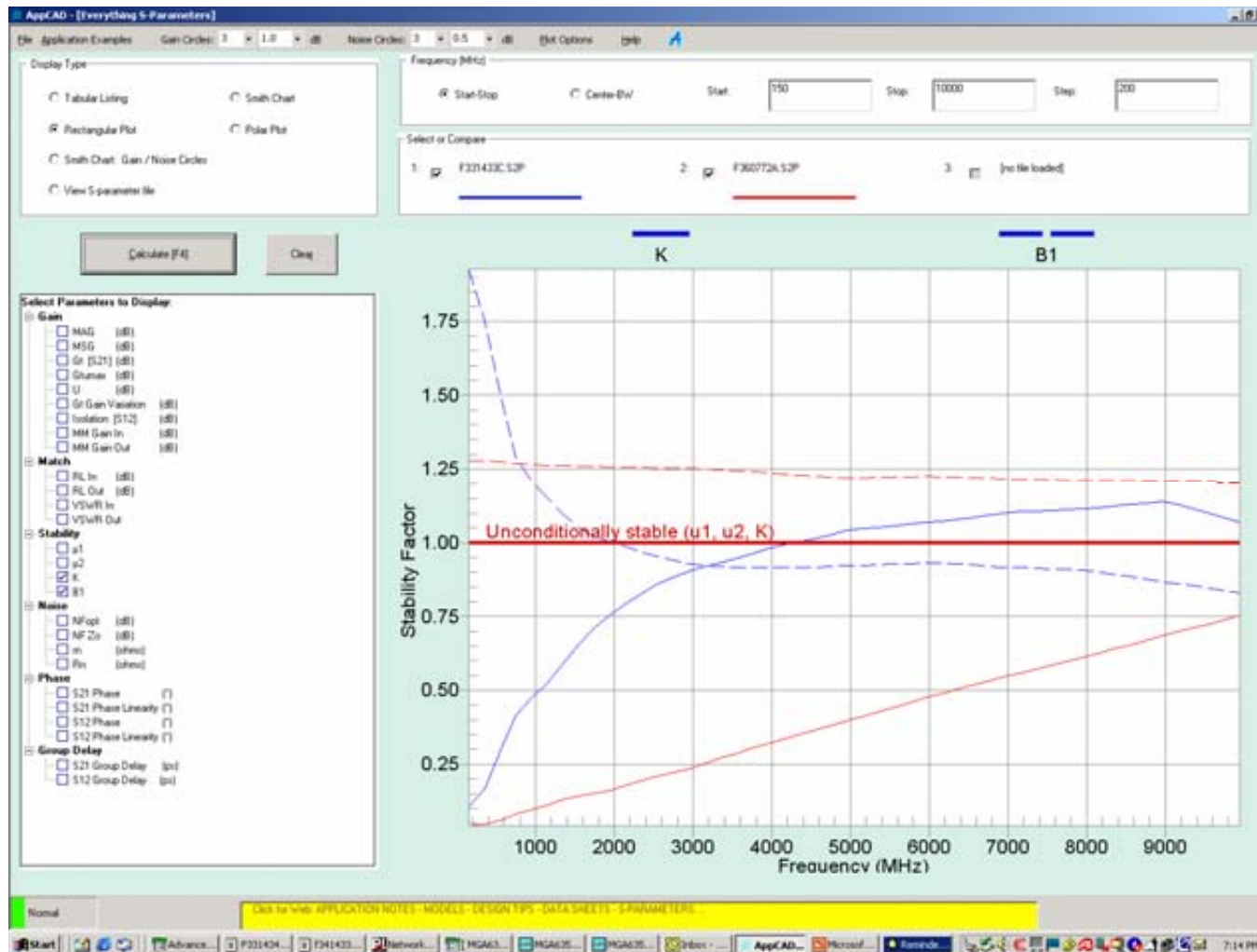
# ATF-36077 vs ATF-33143 Stability Factors vs Freq.



Stability Factor K calculated from S parameters at each frequency,  $K > 1$  for unconditional stability

ATF-36077 –  $K < 1$  at all frequencies below 10 GHz


ATF-33143 –  $K < 1$  only below 4.2 GHz, making the device less sensitive to source grounding – better for VHF LNAs

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |D|^2}{2|S_{12}||S_{21}|}$$

$$D = S_{11}S_{22} - S_{12}S_{21}$$

# ATF-36077 vs ATF-33143

## S21 vs MAG vs MSG


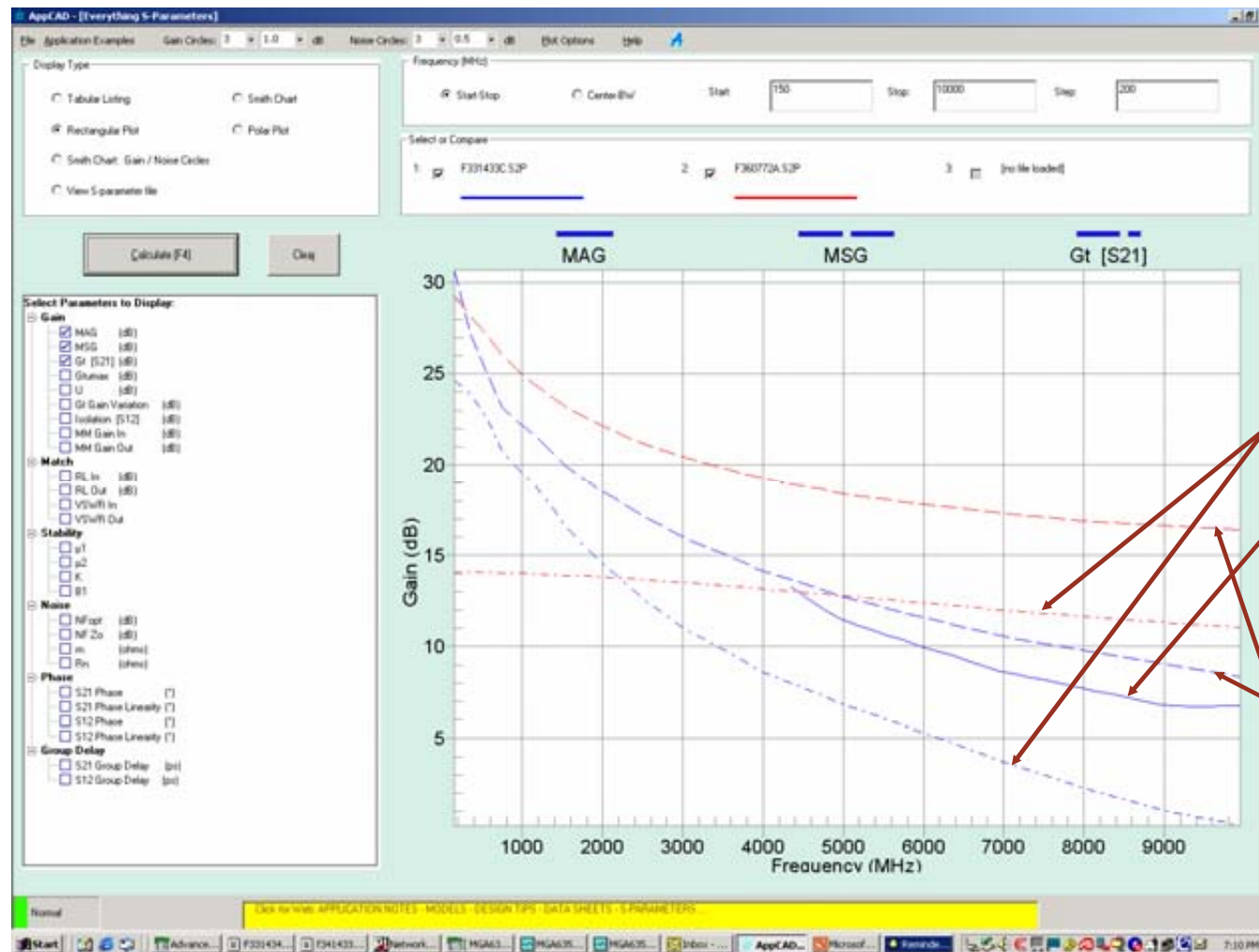


S21 = 50  $\Omega$  Gain

MAG = Maximum Available Gain applies when  $K > 1$

MSG = Maximum Stable Gain


# Contributions to Source Inductance

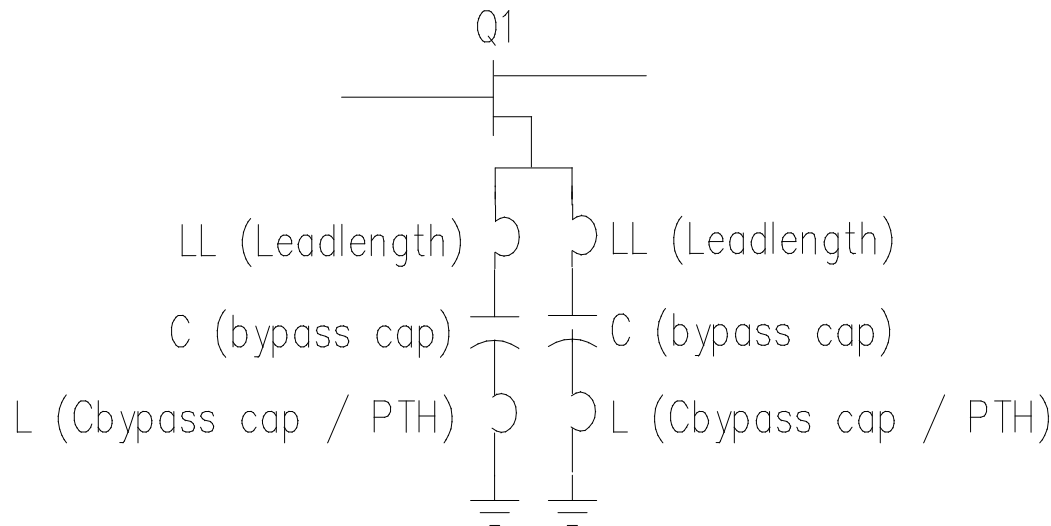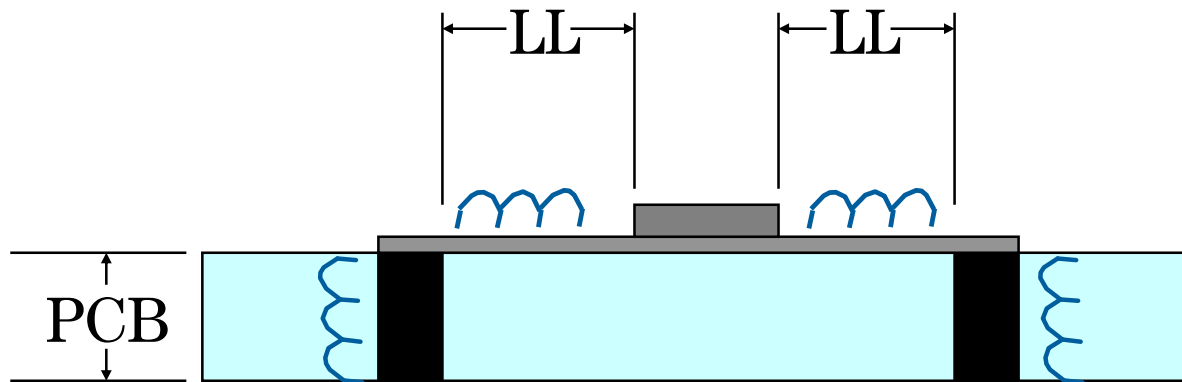


1. Lead length from edge of transistor package to bypass cap or plated through hole adds inductance
2. Use of a source resistor bypass capacitor can alter circuit stability
3. The inductance associated with the bypass capacitor and the equivalent inductance due to the thickness of printed circuit board



# AN 1128 ATF-36077 L Band LNA





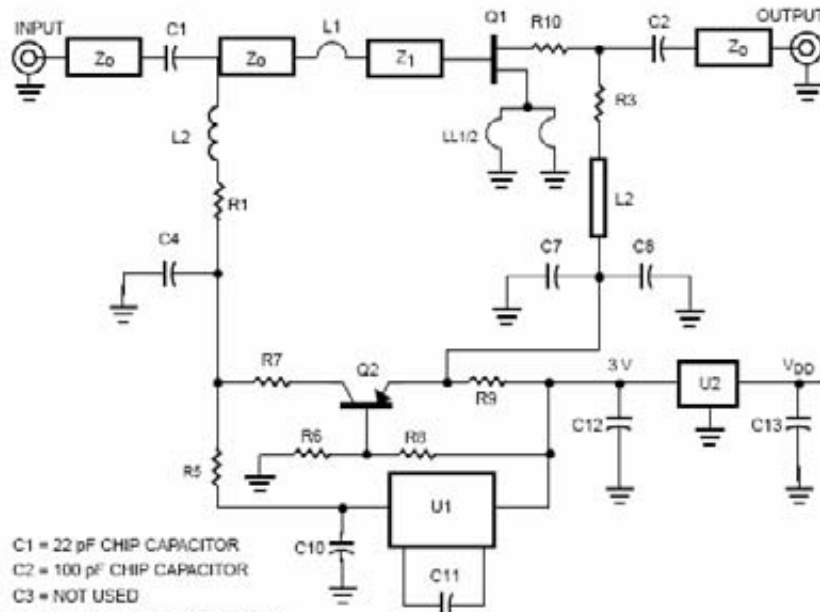


- C1 = 22 pF CHIP CAPACITOR
- C2 = 100 pF CHIP CAPACITOR
- C3 = NOT USED
- C4, C7 = 1000 pF CHIP CAPACITOR
- C5, C6 = NOT USED, GROUND SOURCES DIRECTLY
- C9 = NOT USED
- C8, C12, C13 = 0.1 μF CHIP CAPACITOR
- C10, C11 = 10 μF CHIP CAPACITOR
- L1 = 6T 0.007" DIA. WIRE, 0.050" ID, 0.14" LENGTH
- L2 = 0.18 TO 0.33 μH RFC
- LL1, LL2 = PLATED THROUGH HOLES TO BACKSIDE GROUNDPLANE DIRECTLY UNDER EACH LEAD
- Q1 = AGILENT TECHNOLOGIES ATF-36077 PHEMT
- R1 = 100 OHM CHIP RESISTOR
- R2 = NOT USED
- R3 = 50 OHM CHIP RESISTOR
- R4 = NOT USED
- R5, R7 = 10 k OHM CHIP RESISTOR
- R6 = 1.3 k OHM CHIP RESISTOR
- R8 = 2.7 k OHM CHIP RESISTOR (SETS DRAIN VOLTAGE)
- R9 = 270 OHM CHIP RESISTOR (SETS DRAIN CURRENT)
- R10 = 16 OHM CHIP RESISTOR (UP TO 27 OHMS OK)
- U1 = LINEAR TECHNOLOGY LTC1044CS8 VOLTAGE CONVERTER
- U2 = 5 VOLT REGULATOR TOKO TK11650U

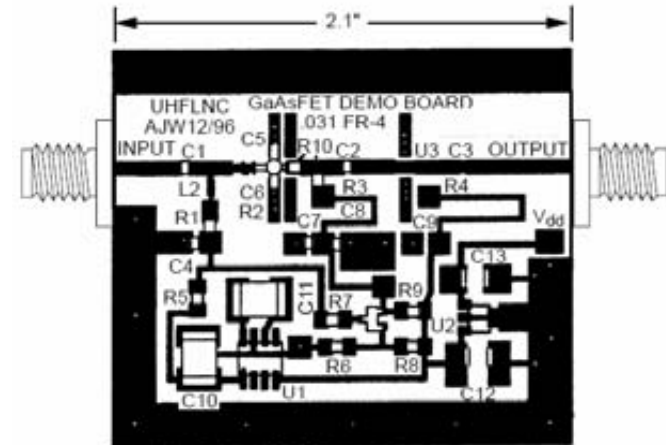


December 1996

# Single stage ATF-36077

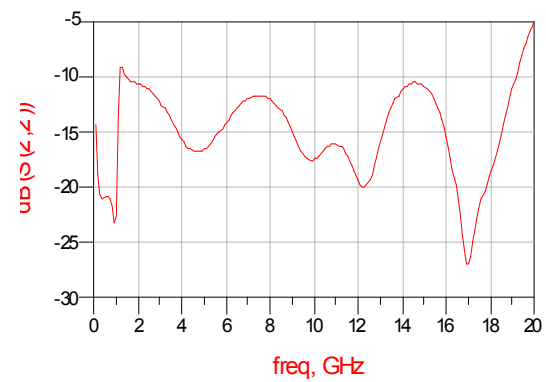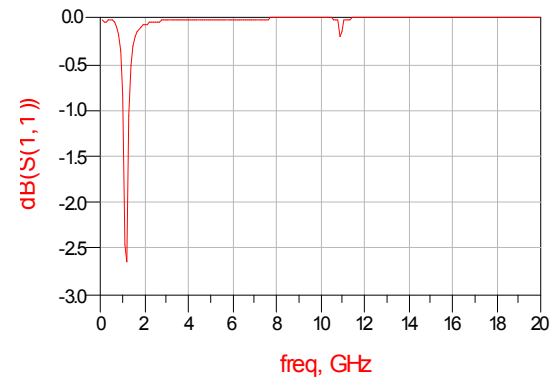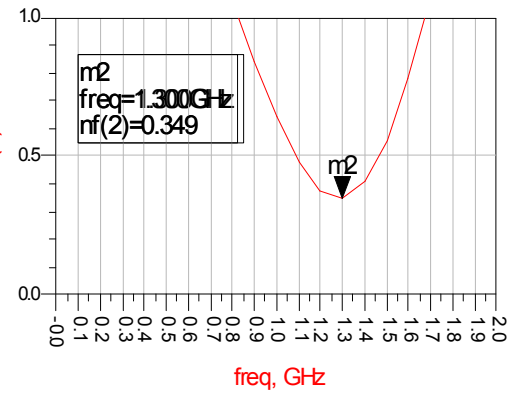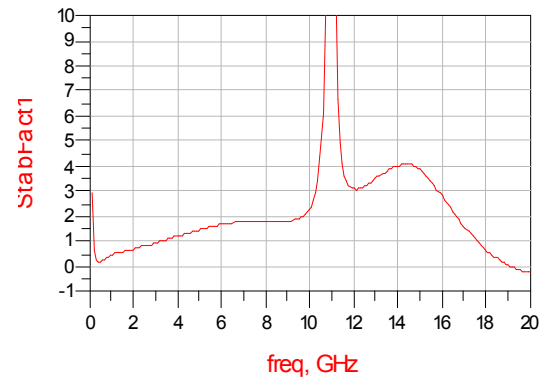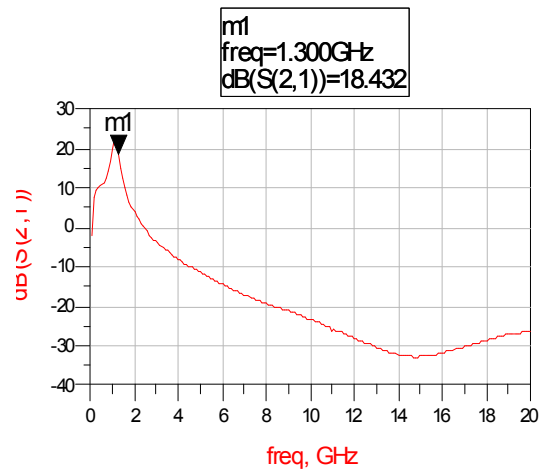

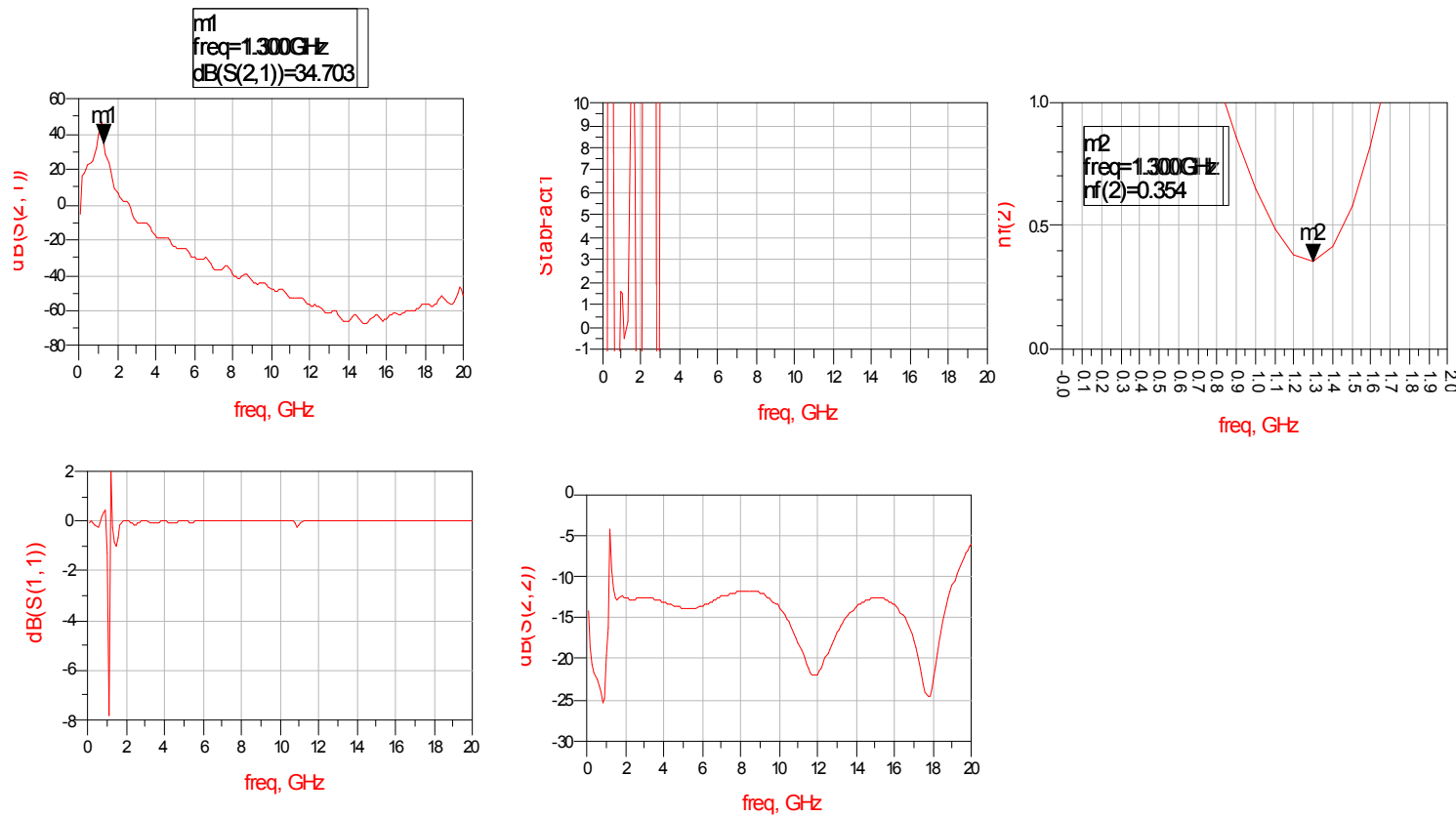
# 2 Stages ATF-36077 Connected with 4.5 inches of 50Ω Coax



Simulation suggests potential stability concerns

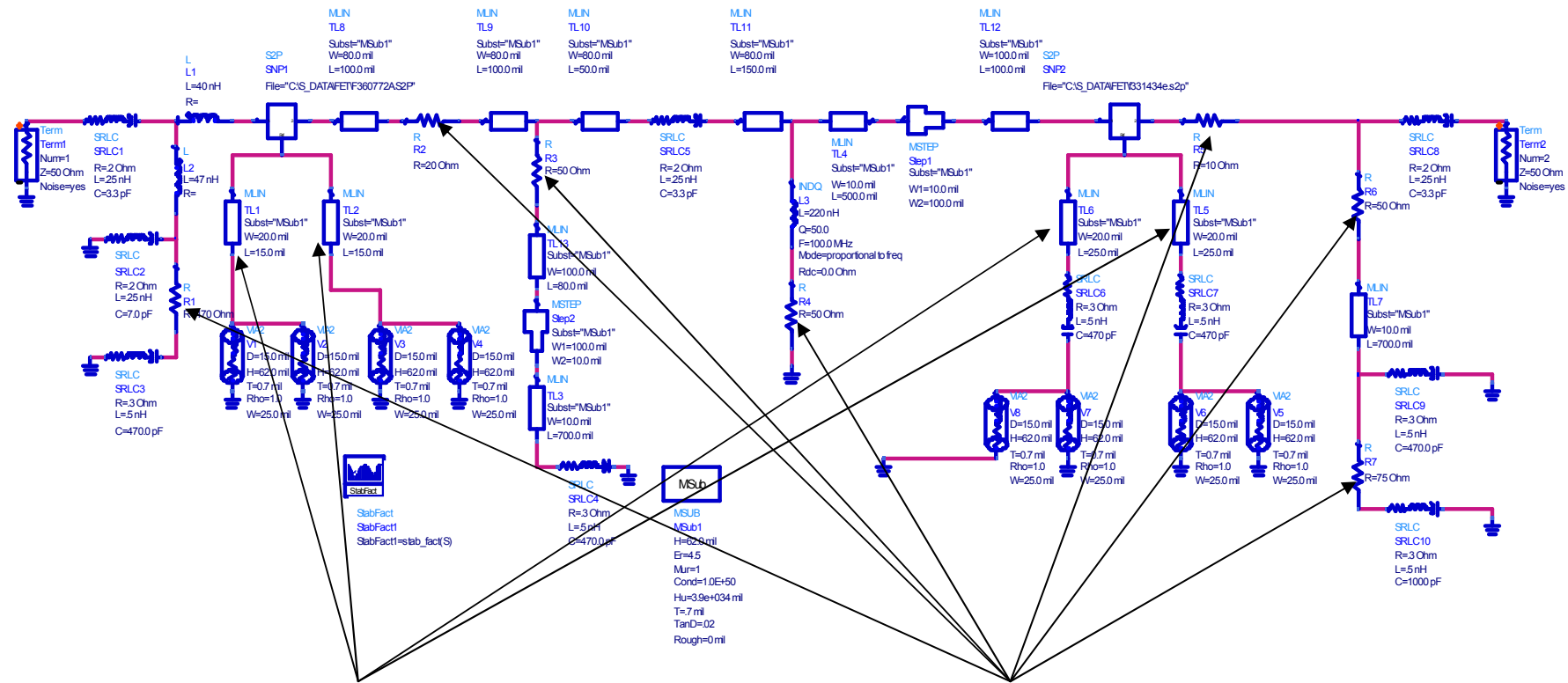
# Better approach is a WD5AGO integrated 2 stage amplifier using an ATF-36077 followed by an ATF-34143 or ATF-54143







Source Inductance

Resistive Loading

# ADS Optimized ATF-36077 First Stage

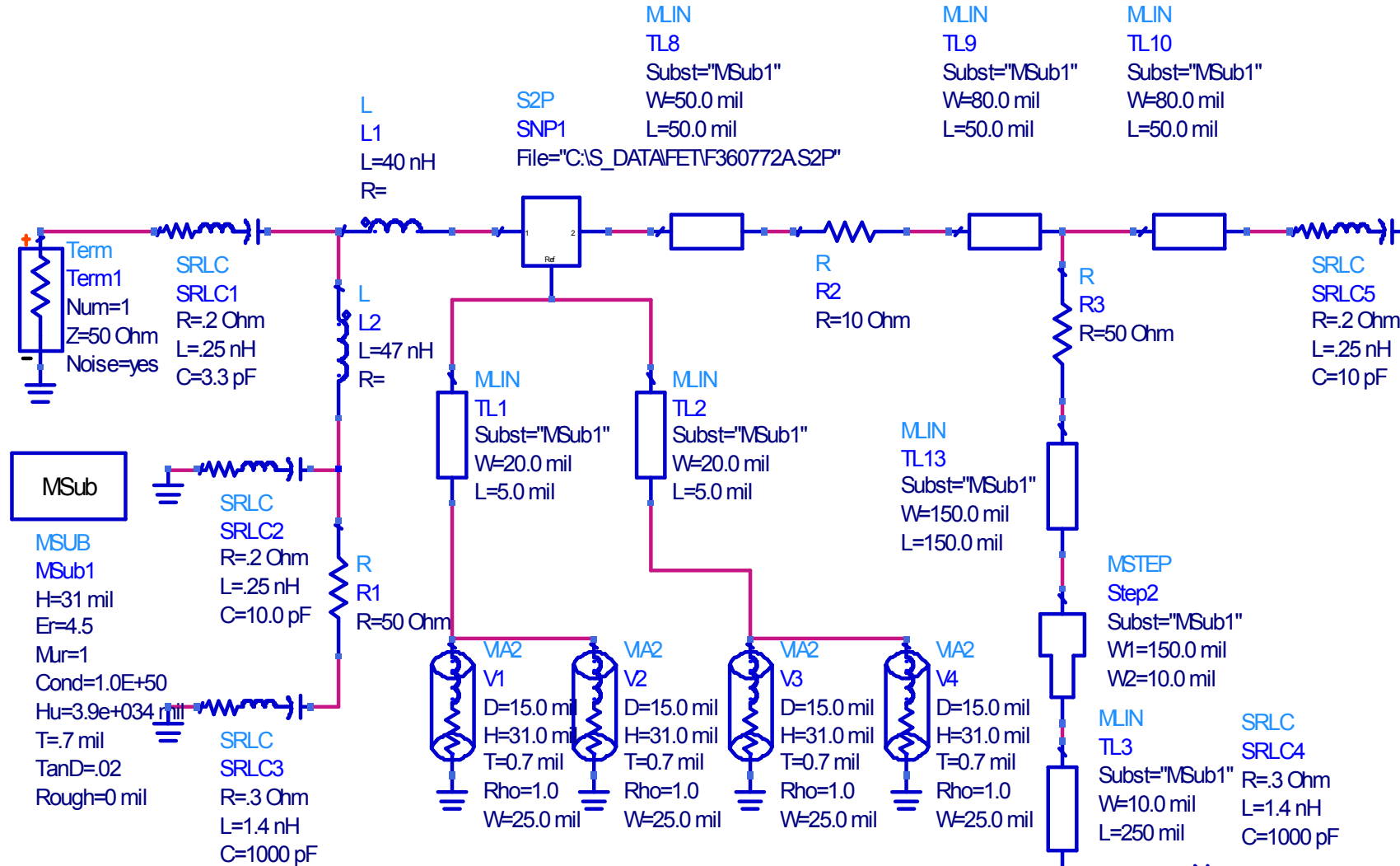

# ADS Optimized ATF-36077 First Stage

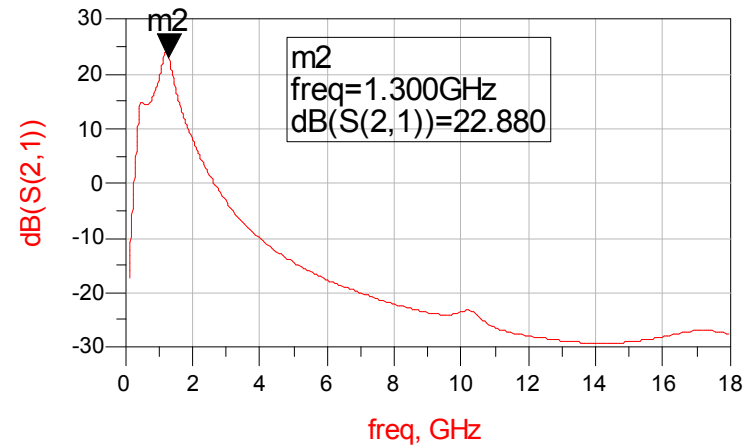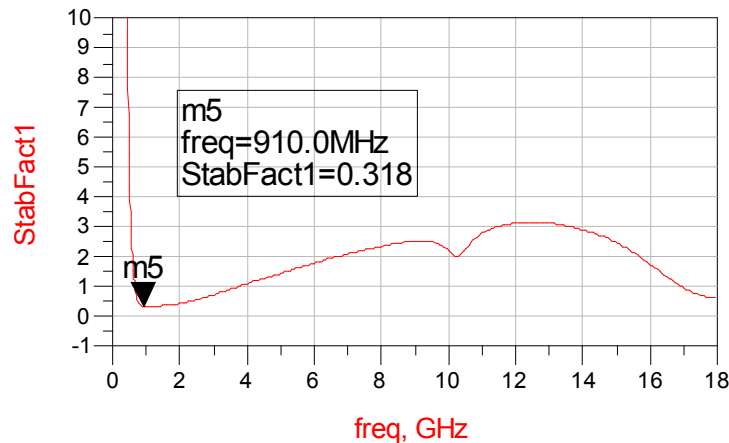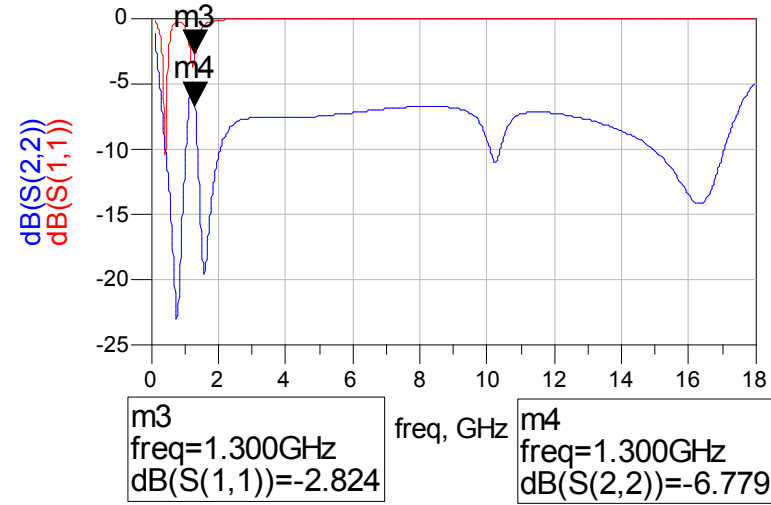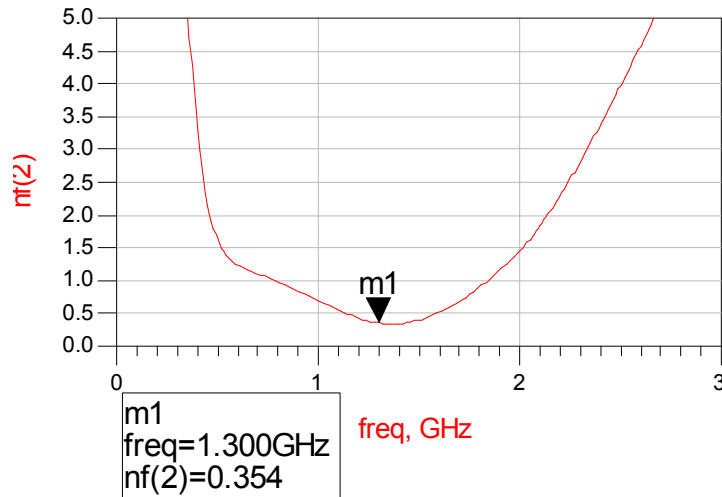

This is about the best that can be had in stability if NF is not to be compromised

## Let's take a look at second stage candidates

**ATF-36077 200 u gate width depletion mode device**





**ATF-21186 750 u gate width depletion mode device**

**ATF-33143 800 u gate width depletion mode device**

**ATF-54143 400 u gate width enhancement mode device**


**Other candidates**

# Optimized ATF-54143 Second Stage

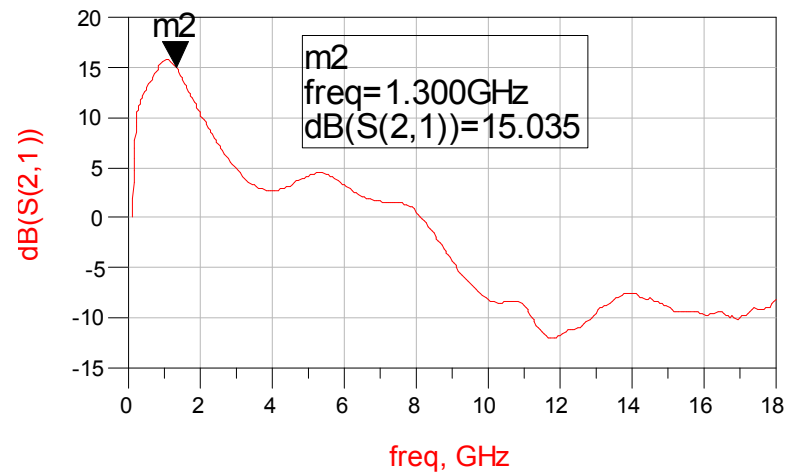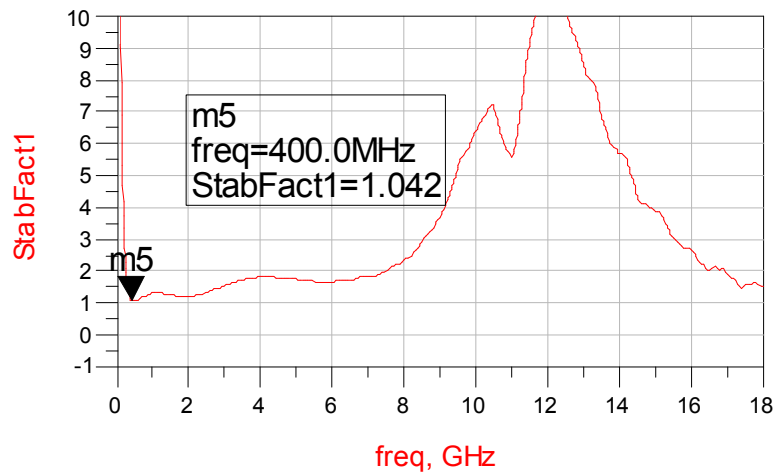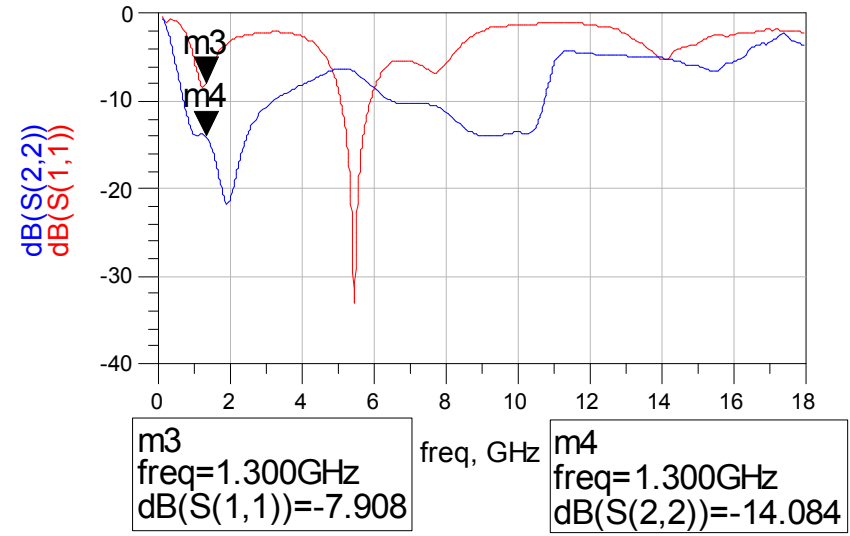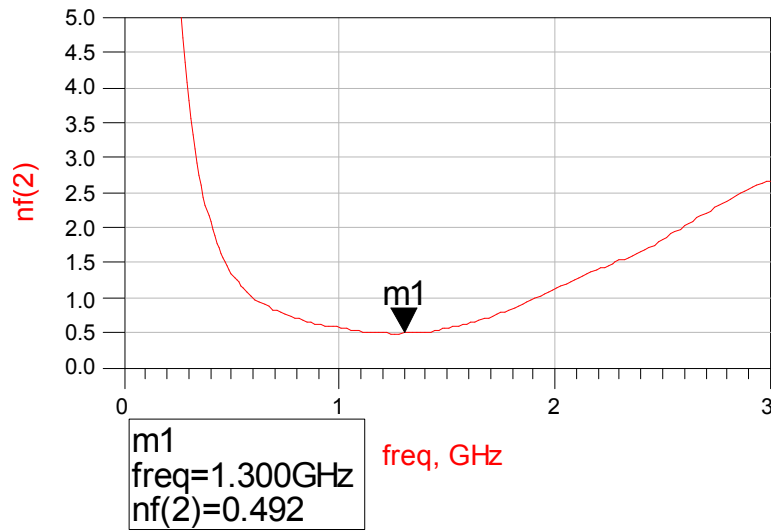





# Optimized ATF-54143 Second Stage

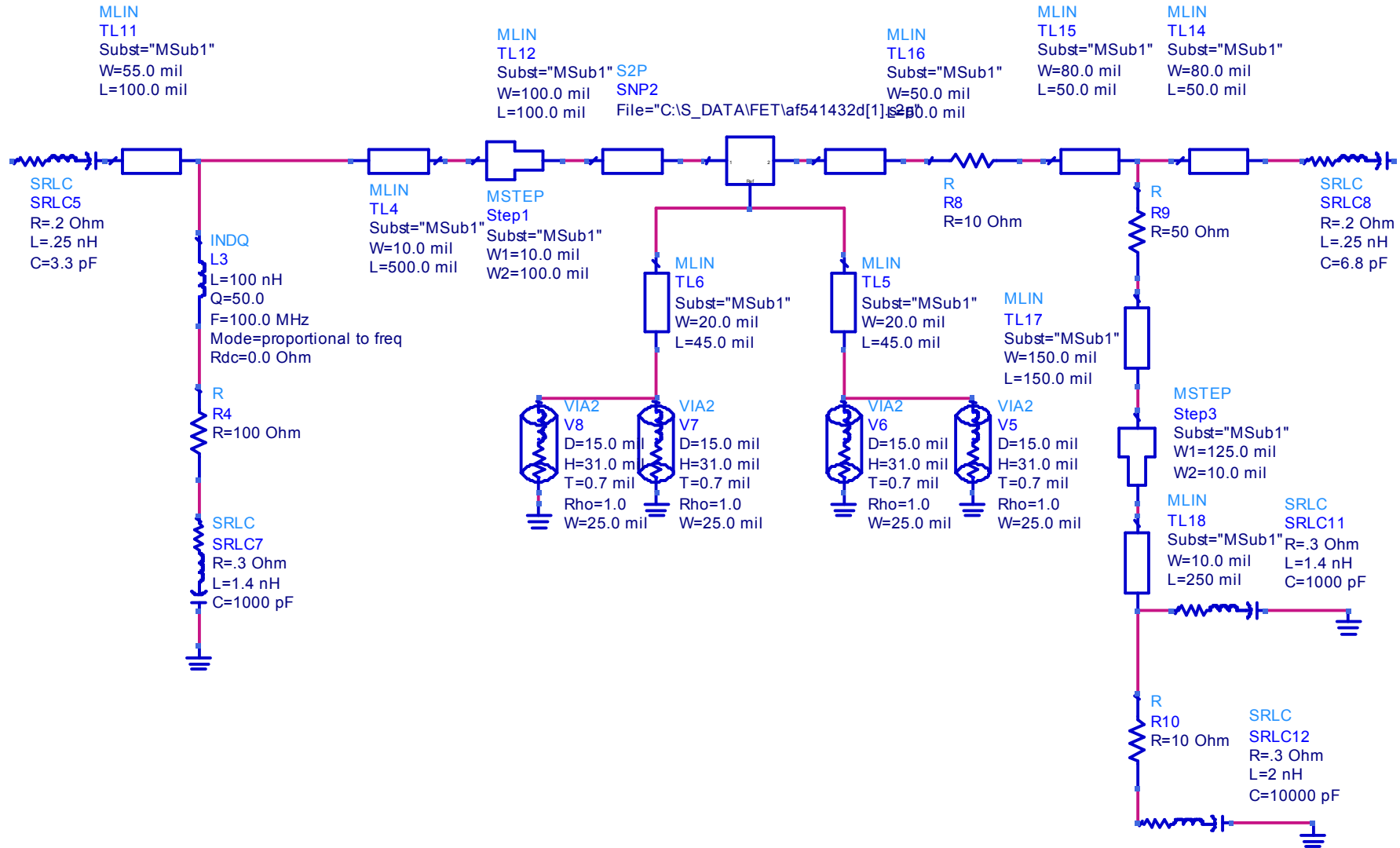

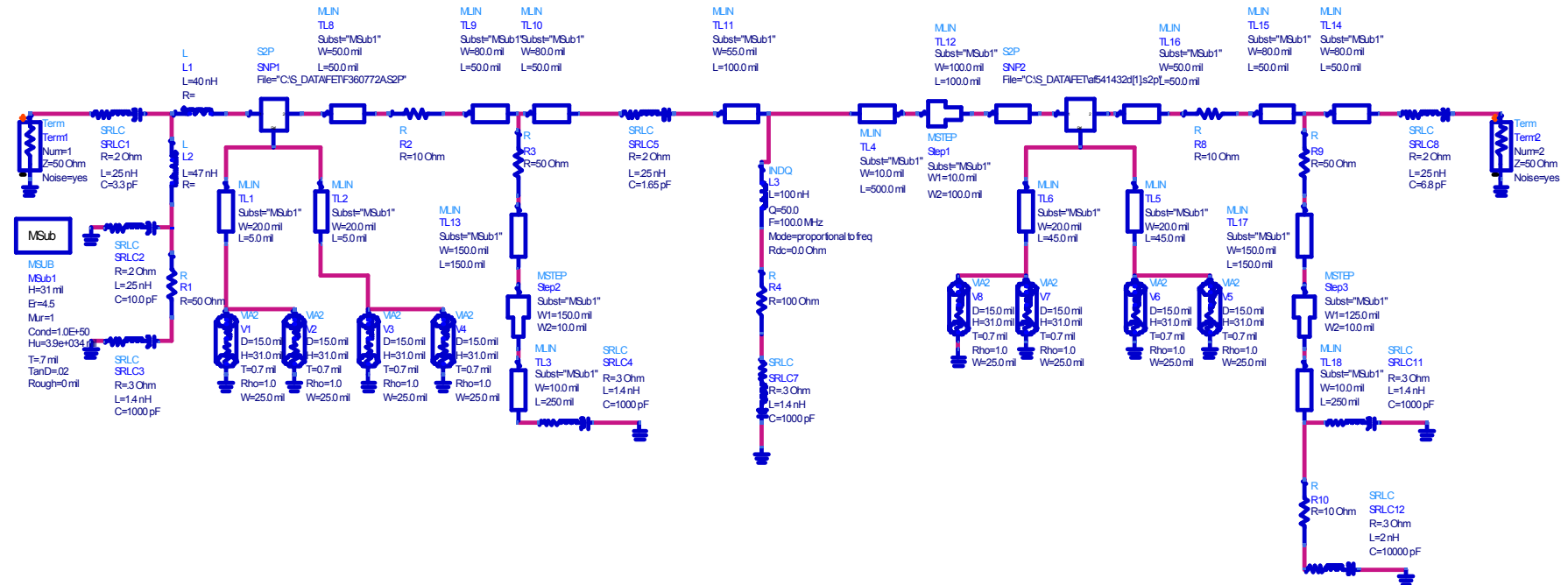
# ATF-36077 cascaded with improved ATF-54143 Second Stage


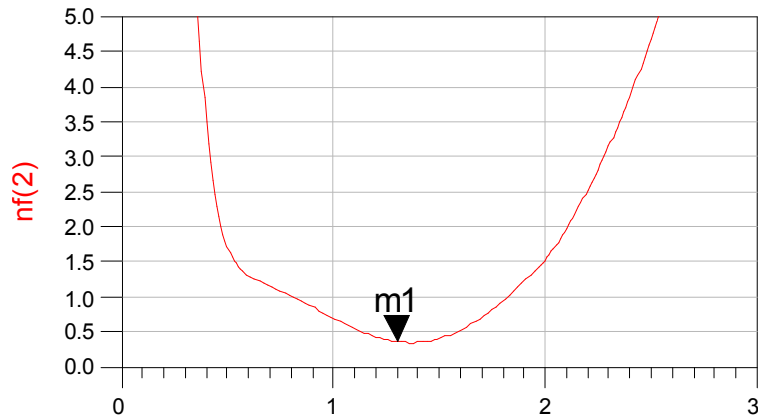
# ATF-36077 cascaded with improved ATF-54143 Second Stage




m1  
freq=1.300GHz  
nf(2)=0.359

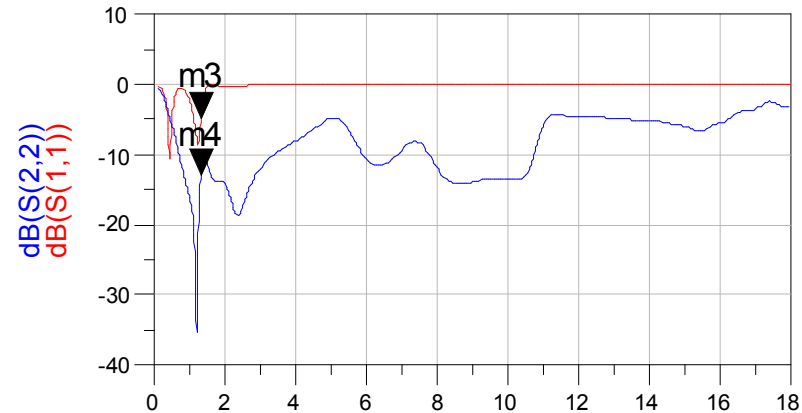


m3  
freq=1.300GHz  
dB(S(1,1))=-4.904

m4  
freq=1.300GHz  
dB(S(2,2))=-12.991

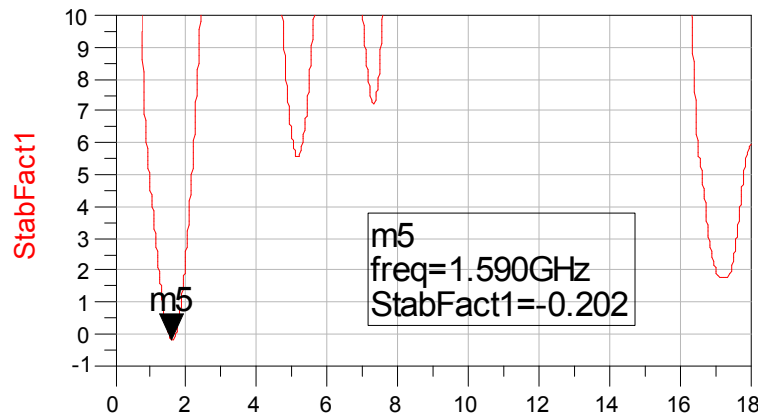


m5  
freq=1.590GHz  
StabFact1=-0.202

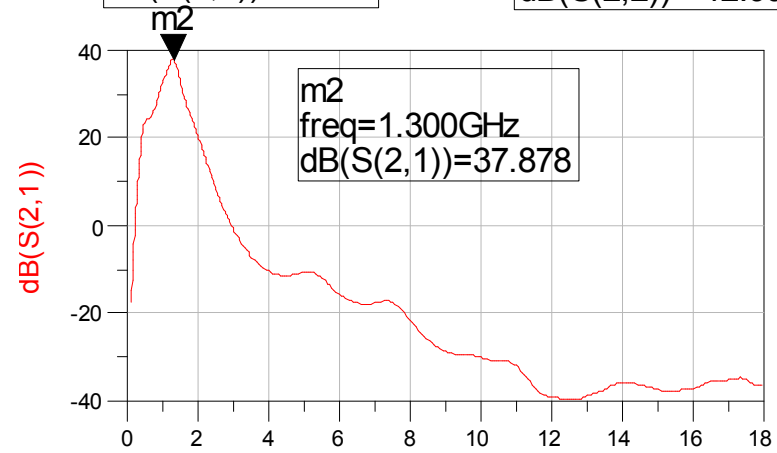


m2  
freq=1.300GHz  
dB(S(2,1))=37.878

Still some concern about stability

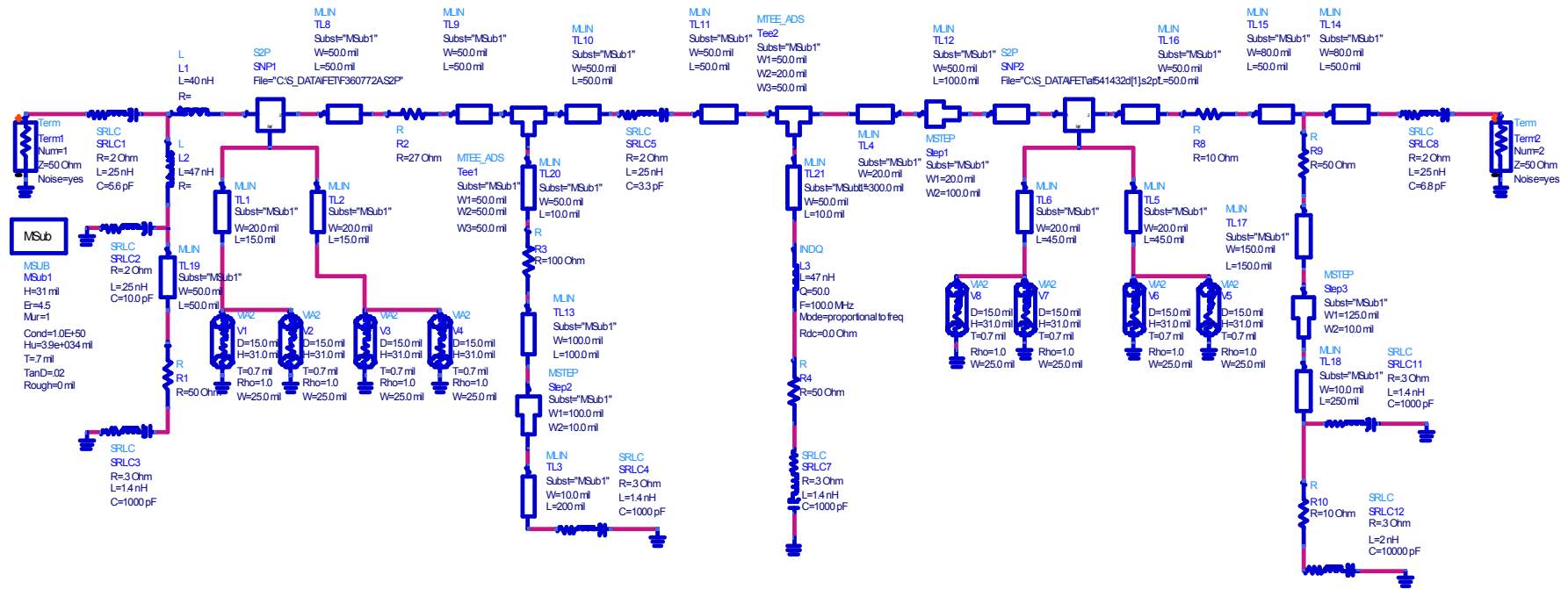
# ATF-36077 ATF-54143 Cascade with Further Improvements


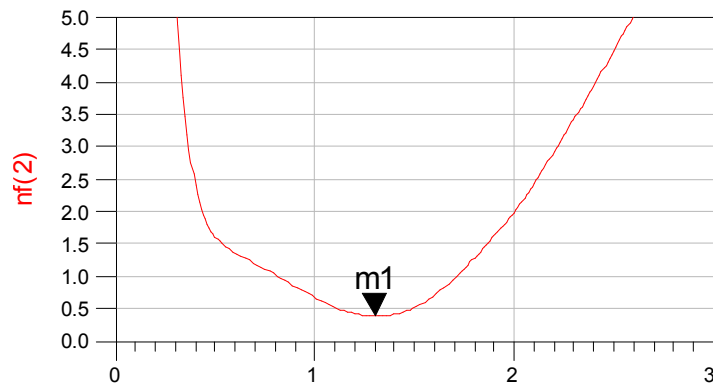
# ATF-36077 ATF-54143 Cascade with Further Improvements




m1  
freq=1.300GHz  
nf(2)=0.377

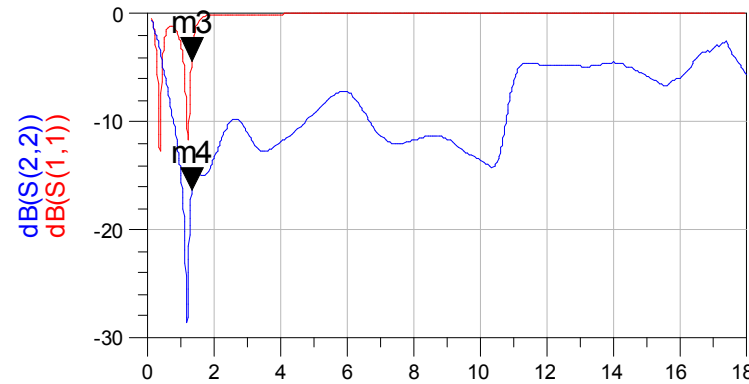


m3  
freq=1.300GHz  
dB(S(1,1))=-4.413

m4  
freq=1.300GHz  
dB(S(2,2))=-16.431

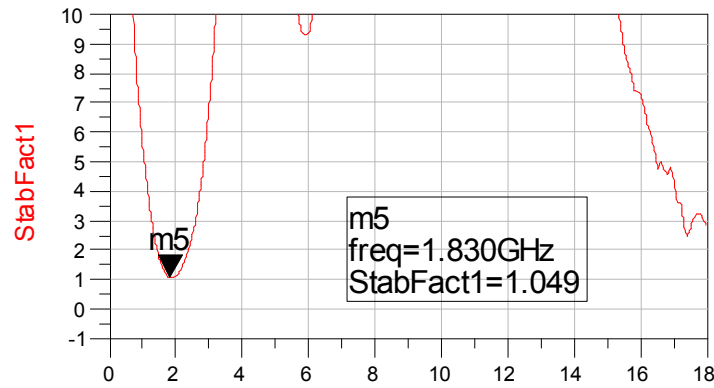

m5  
freq=1.830GHz  
StabFact1=1.049

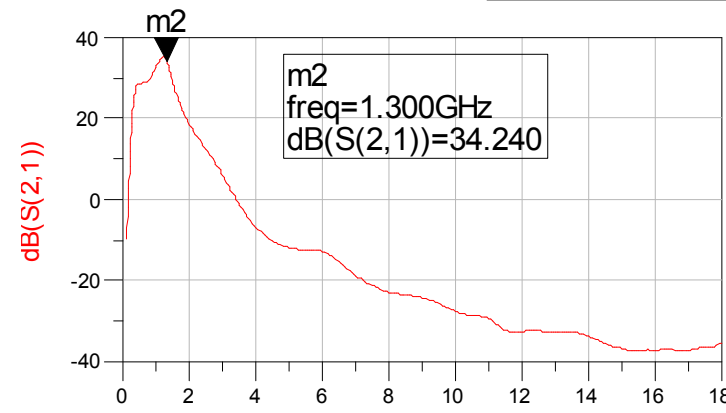

m2  
freq=1.300GHz  
dB(S(2,1))=34.240

At this point  $R_d = 27$  ohms to get  $K=1$  but  $NF .377$ . This is the best that can be done with ATF-36077 driving ATF-54143....


## What would make a better second stage?

**Maybe a MMIC**


**The WLAN and WiMAX markets have forced semiconductor manufacturers to build sub 1 dB noise figure MMICs – these might make a good second stage but..**

**Most are in nasty little hard to see packages with no leads except maybe the MGA-61563.....**

# Effects of 2<sup>nd</sup> Stage

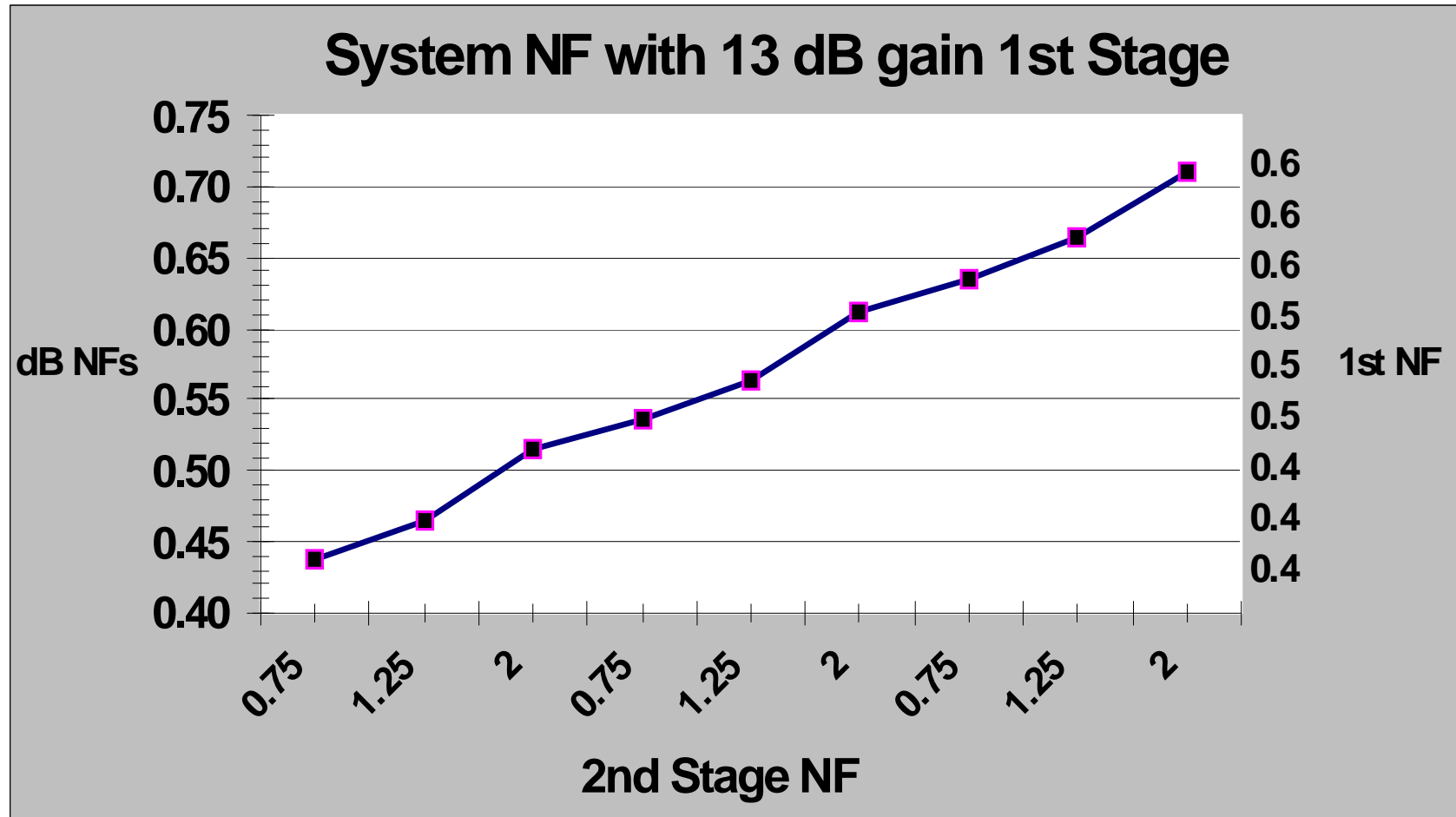


# MGA-61563 Low Noise Amplifier

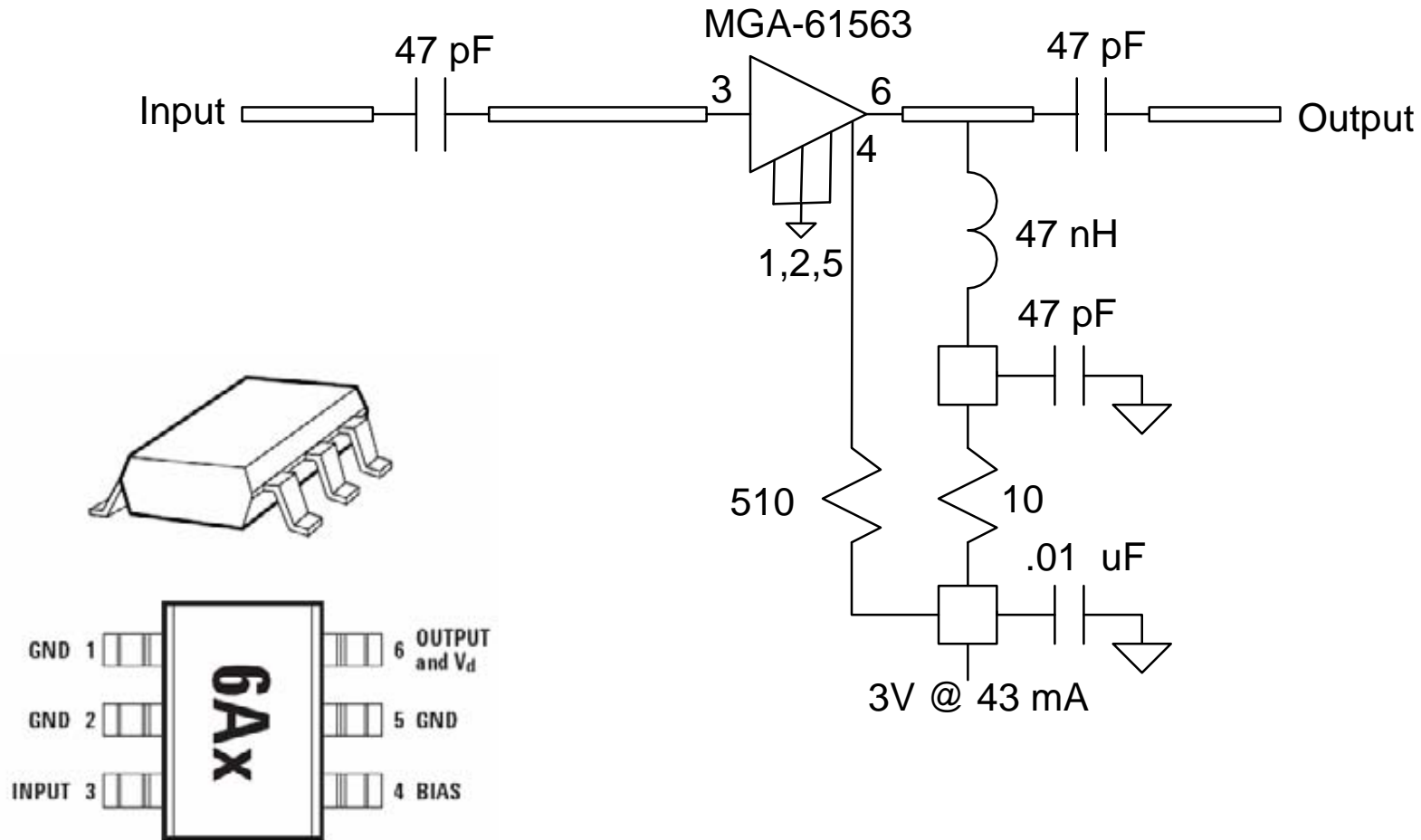



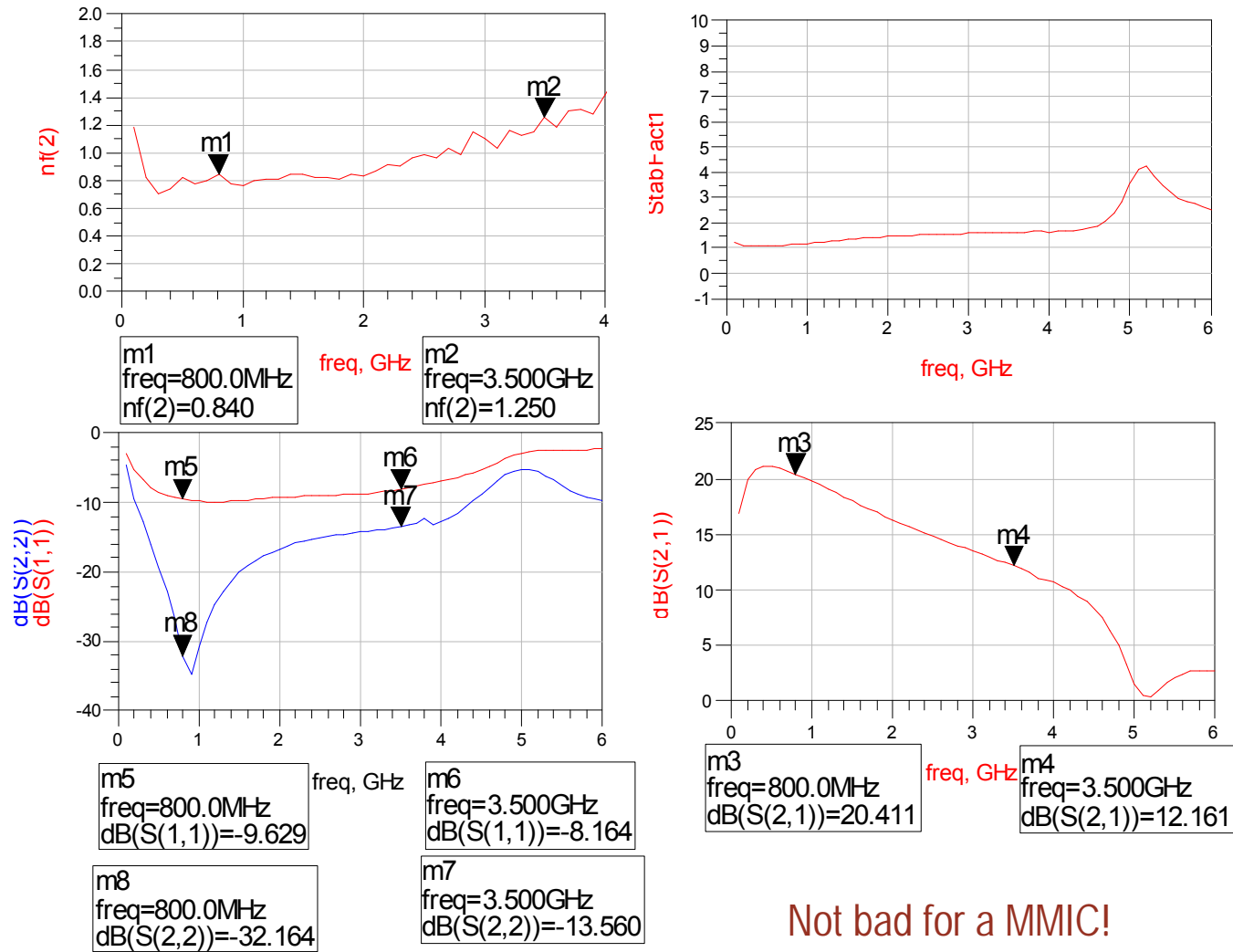
# MGA-61563 Measured Demo Board Performance




Not bad for a MMIC!
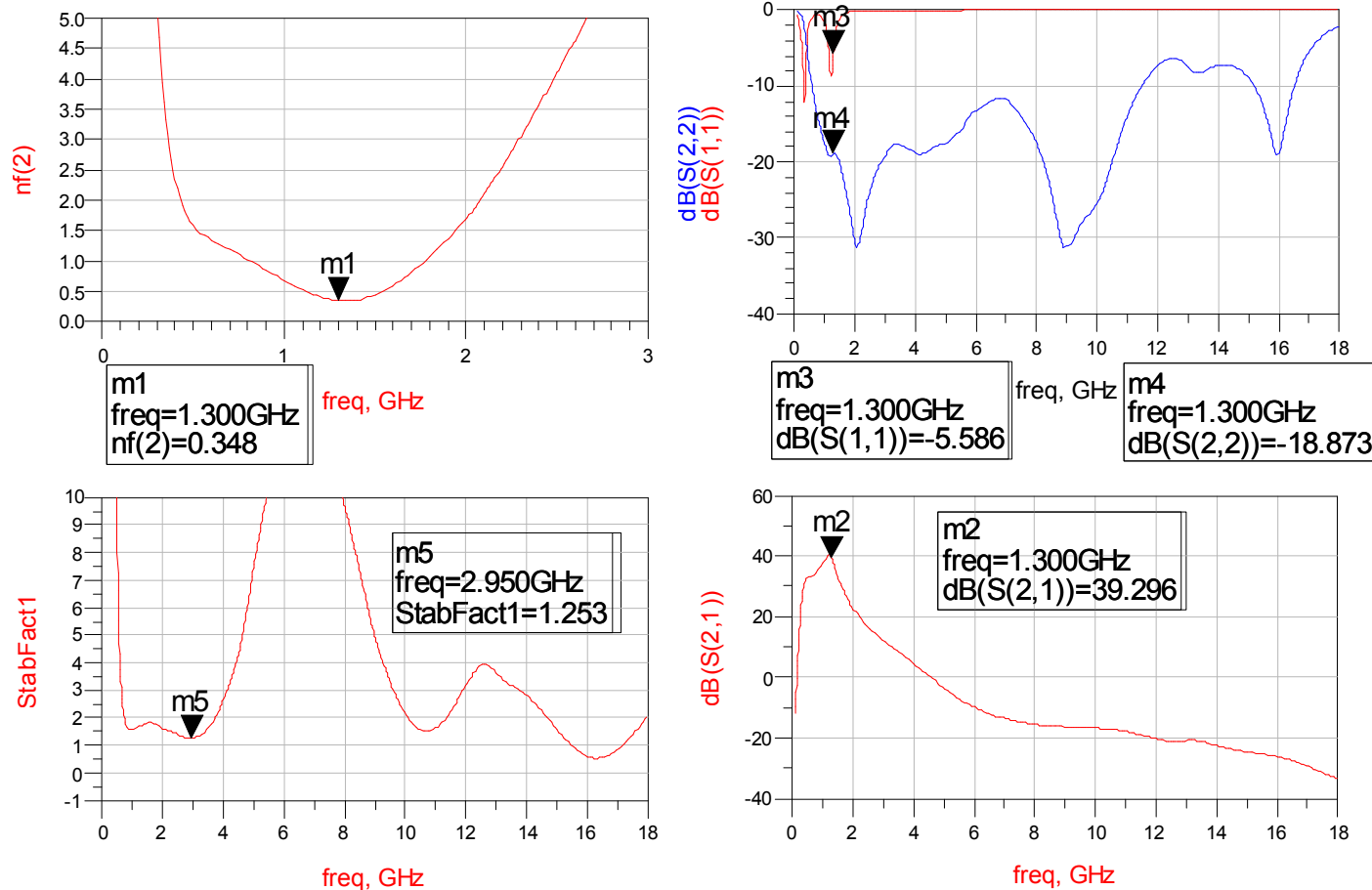
# ADS Simulation with ATF-36077 MGA-61563 Cascade




I don't believe K is a problem at 16 GHz but if it is a little Rd will help
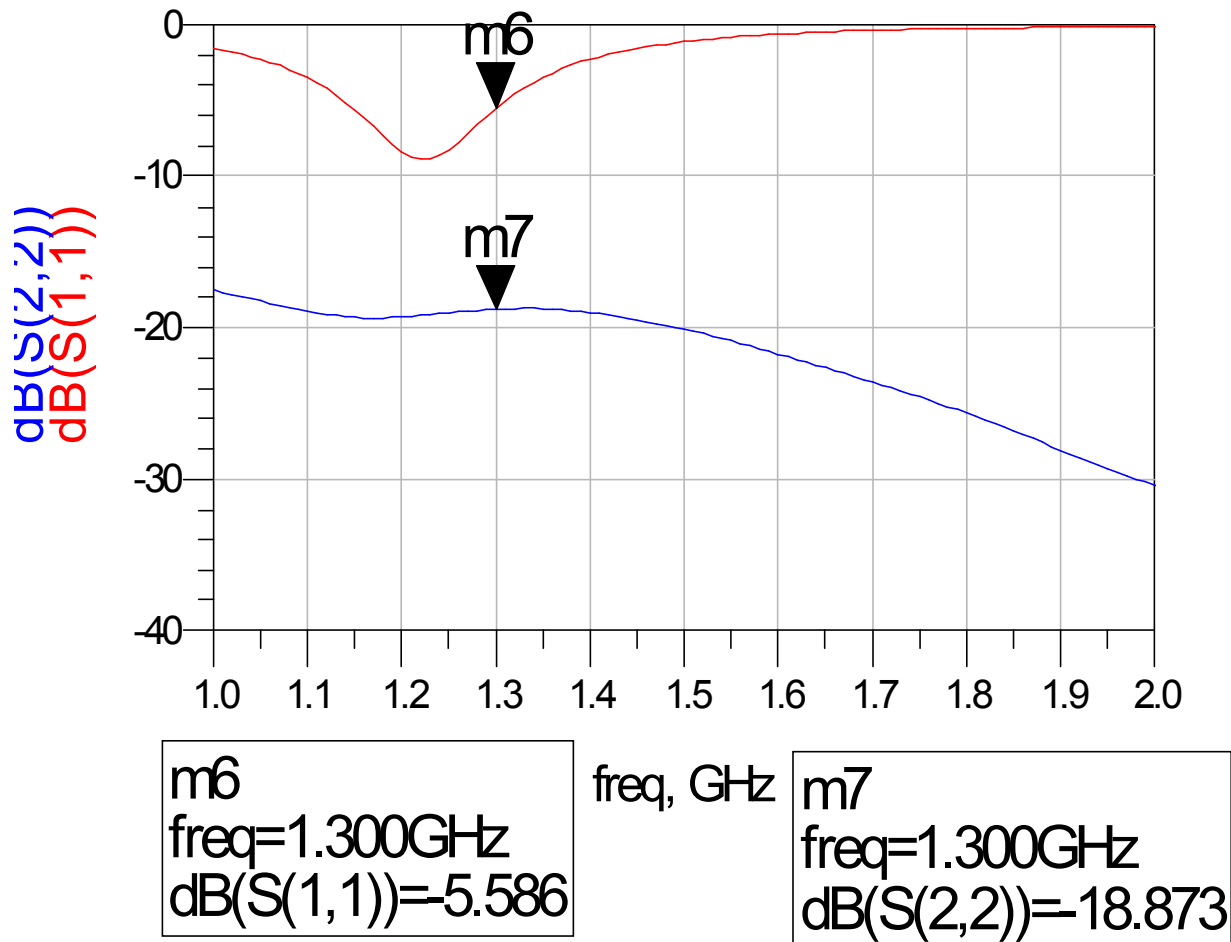
# ADS Simulation with ATF-36077 MGA-61563 Cascade




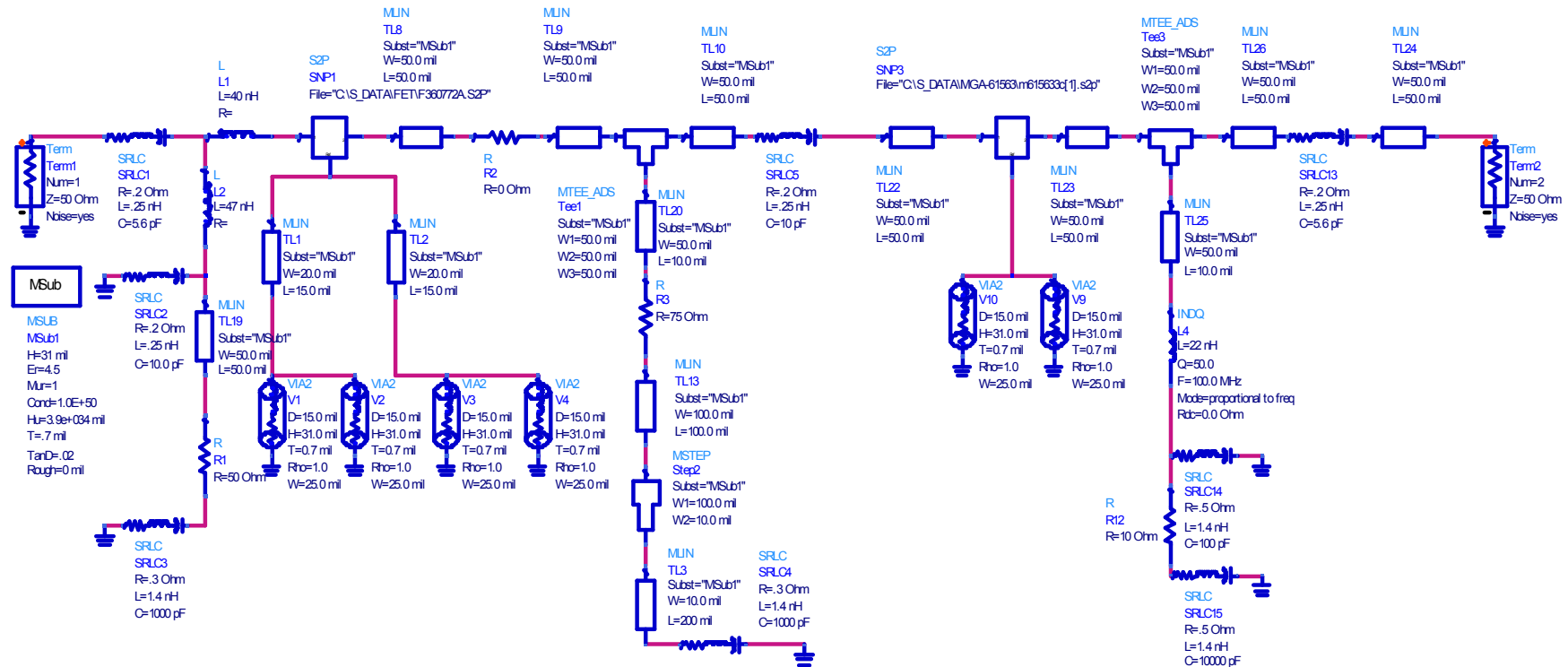
# ADS Simulation with ATF-36077 MGA-61563 Cascade







This is the approach taken for a new WD5AGO LNA

## 2 Stage ATF-36077 & MGA-61563 LNA



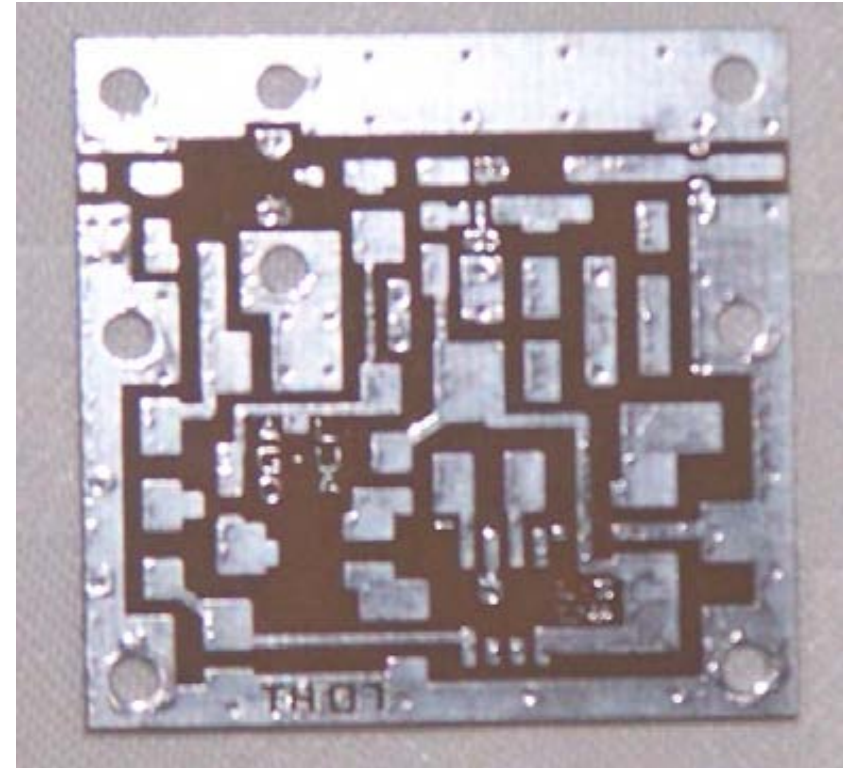
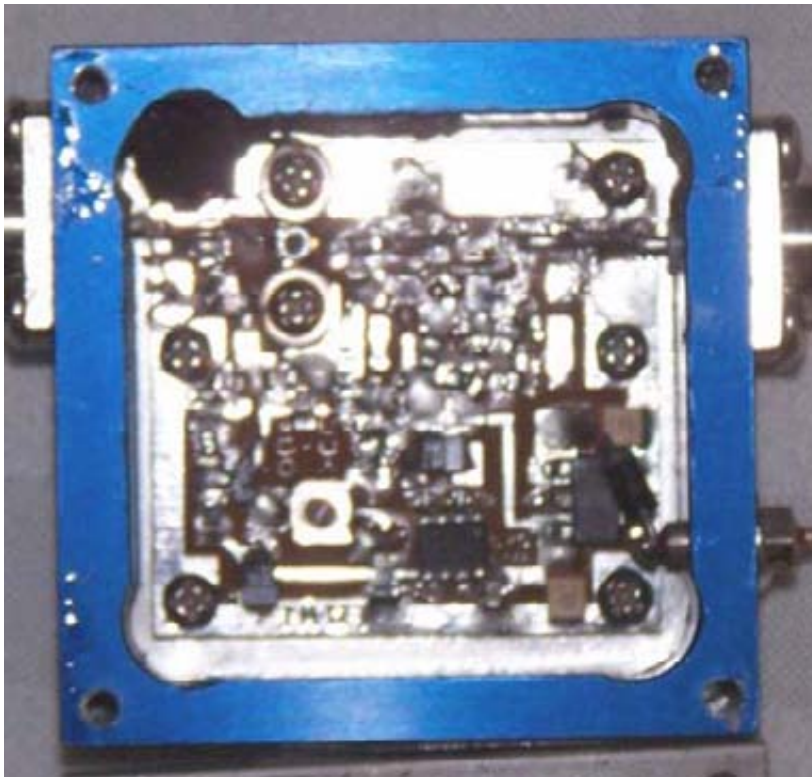

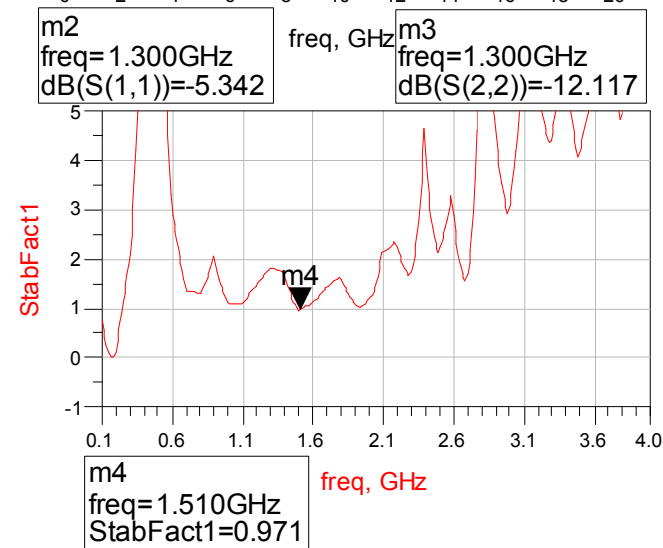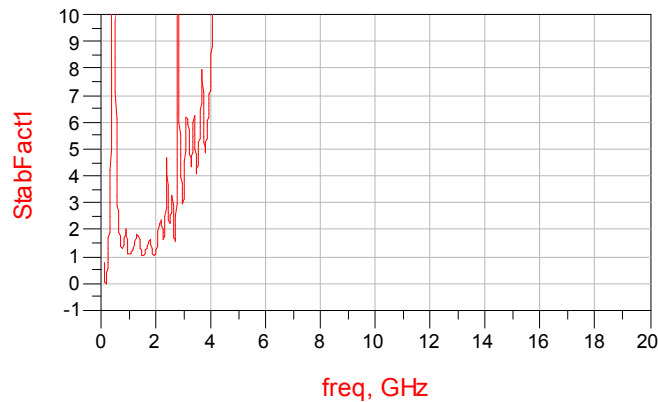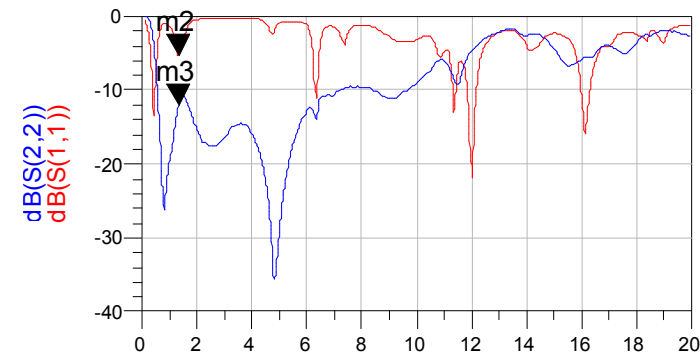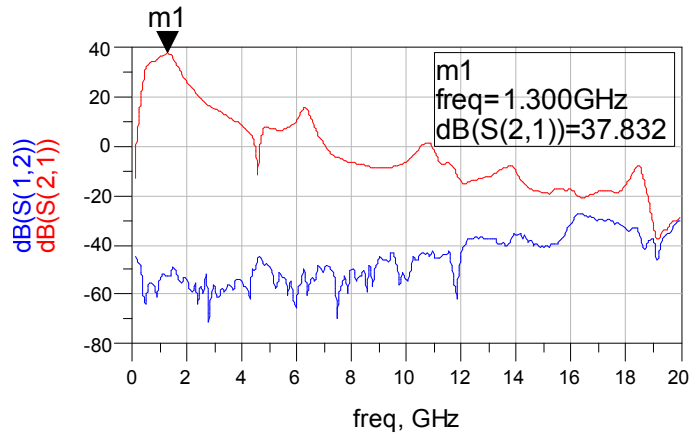
## 2 Stage ATF-36077 & MGA-61563 #1 Measured Results




NF measured 0.35 dB at 1296 MHz. K at low frequency erroneous due to lack of S12 due to poor dynamic range in test equipment. Tough when LNA has 37 dB gain!

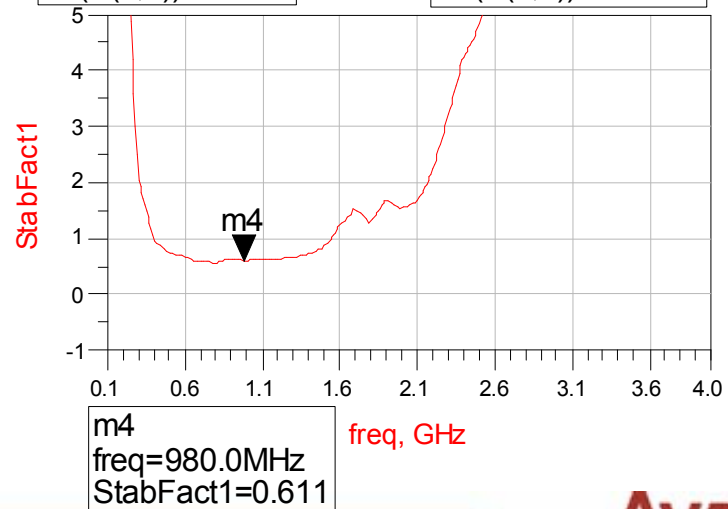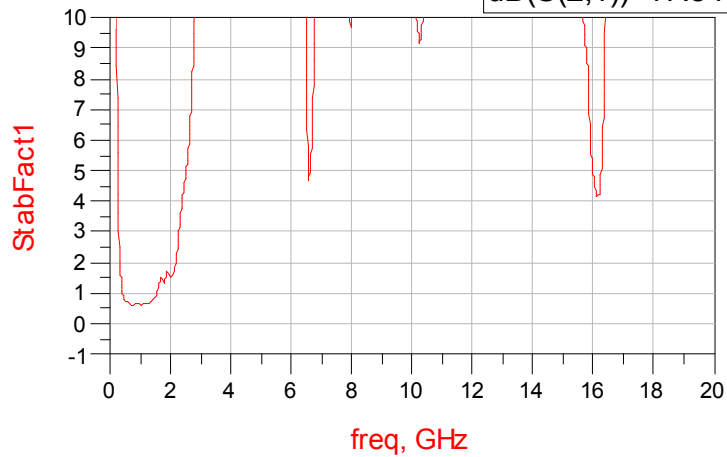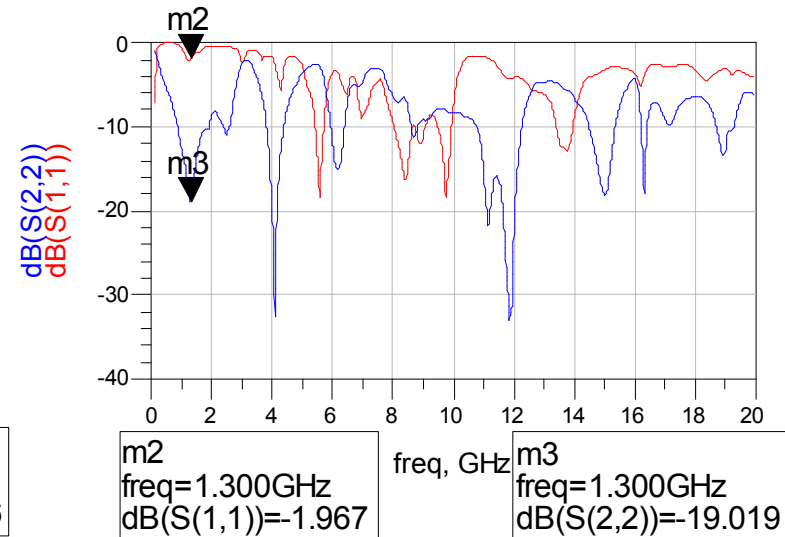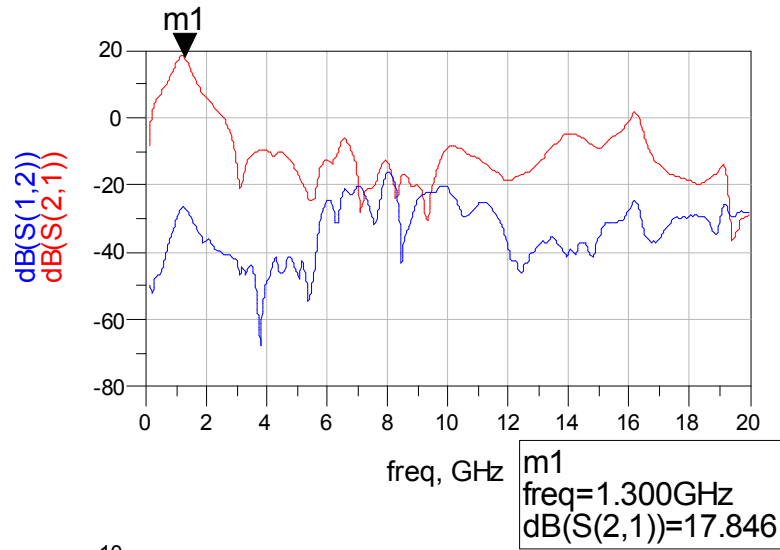
# AP Note 1228 Single Stage ATF-36077 Measured Results


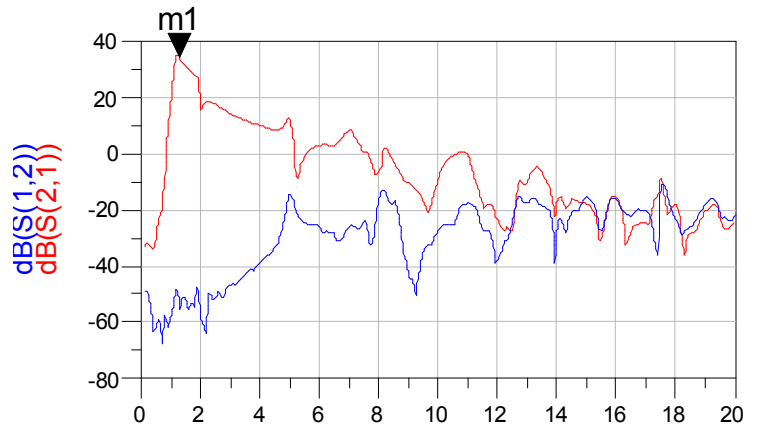
# 2 Stage ATF-36077 & MGA-61563 in Enclosure





m1  
freq=1.300GHz  
dB(S(2,1))=34.240

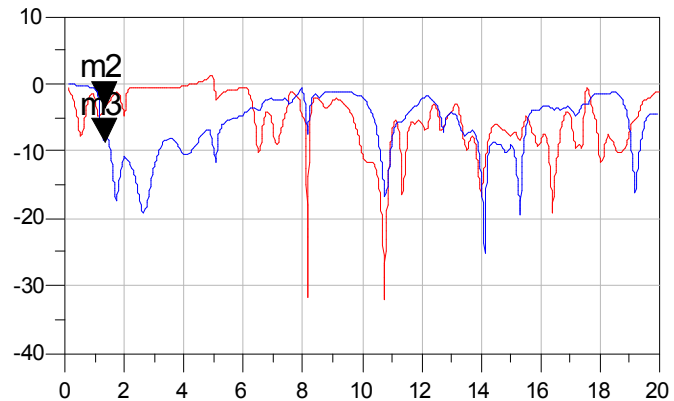

m2  
freq=1.300GHz  
dB(S(1,1))=-3.452





m3  
freq=1.300GHz  
dB(S(2,2))=-8.710

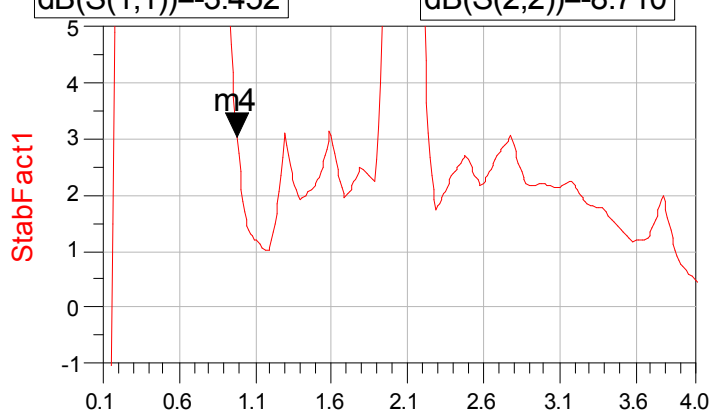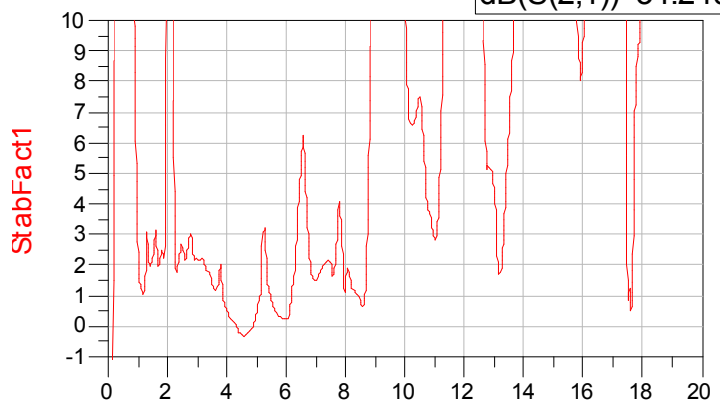




m4  
freq=980.0MHz  
StabFact1=3.027


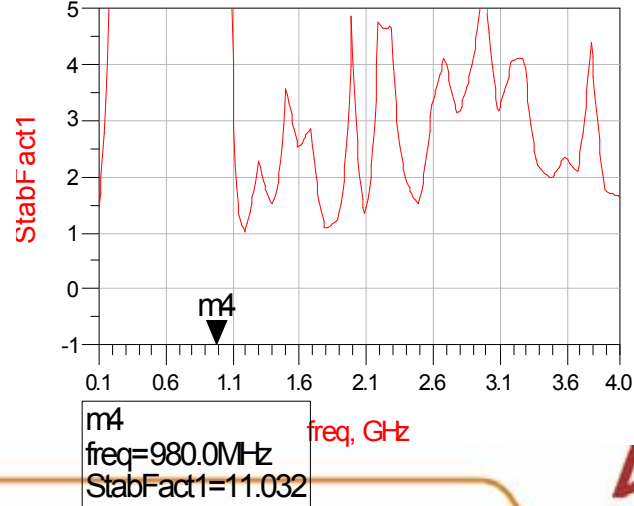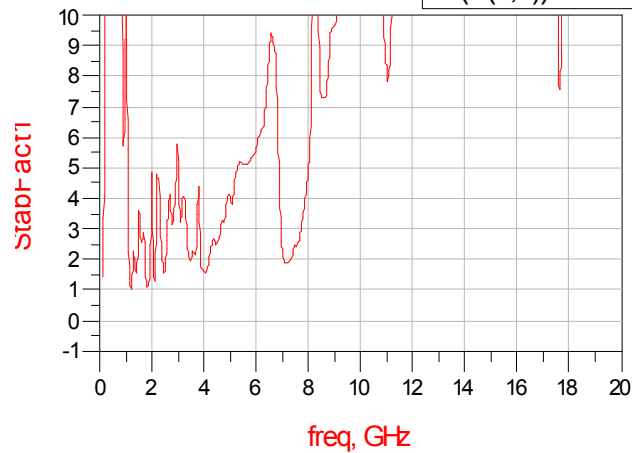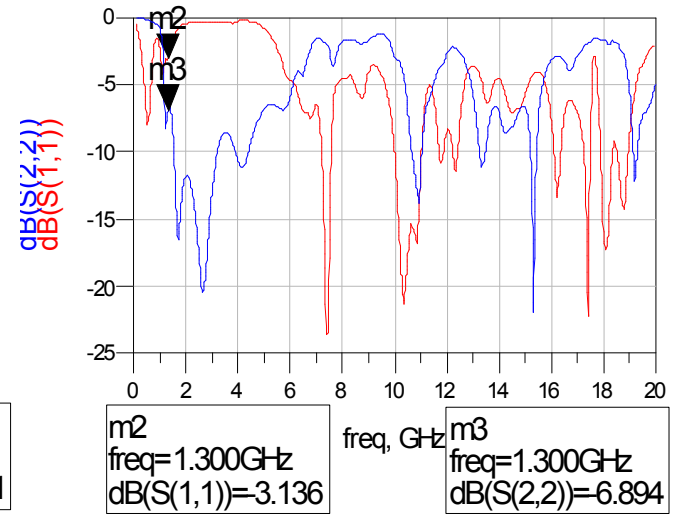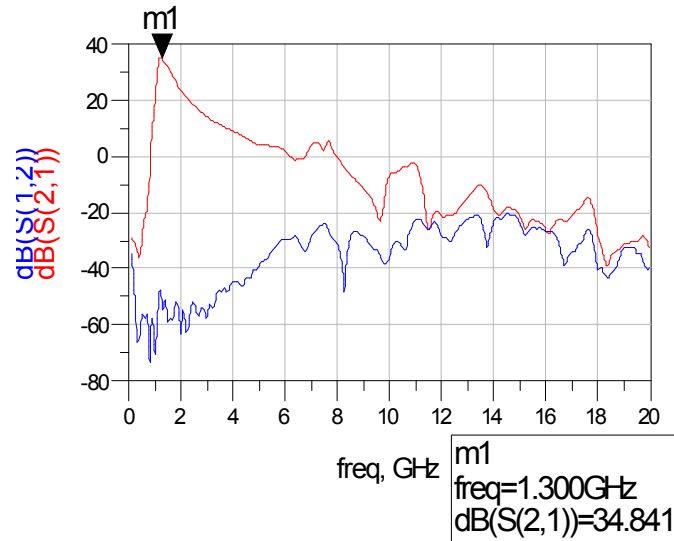
# 2 Stage ATF-36077 & MGA-61563 in Enclosure without Lid







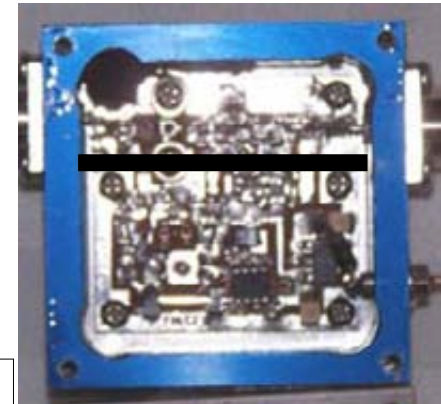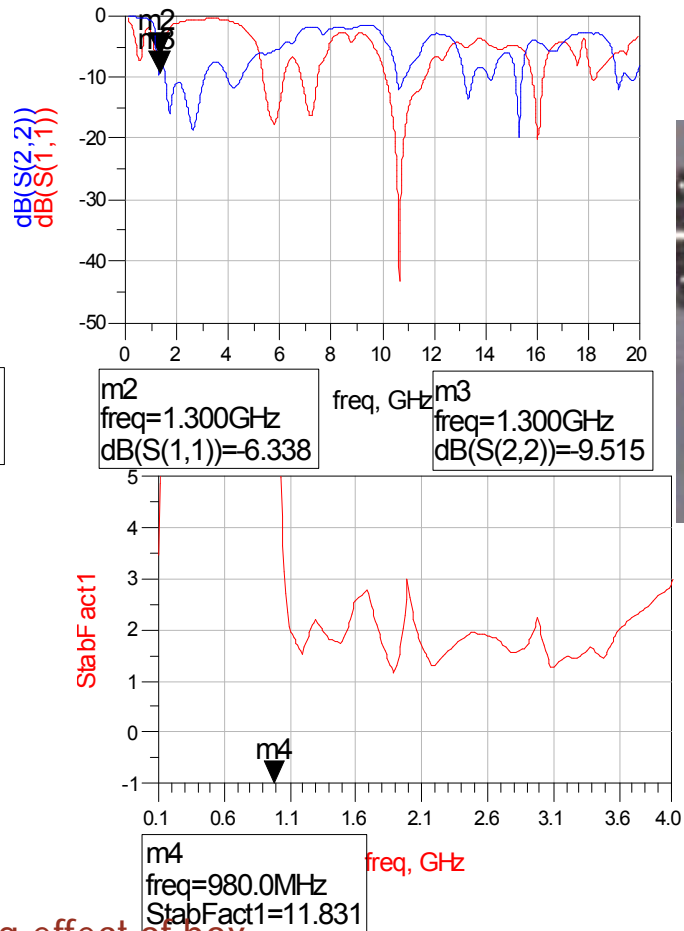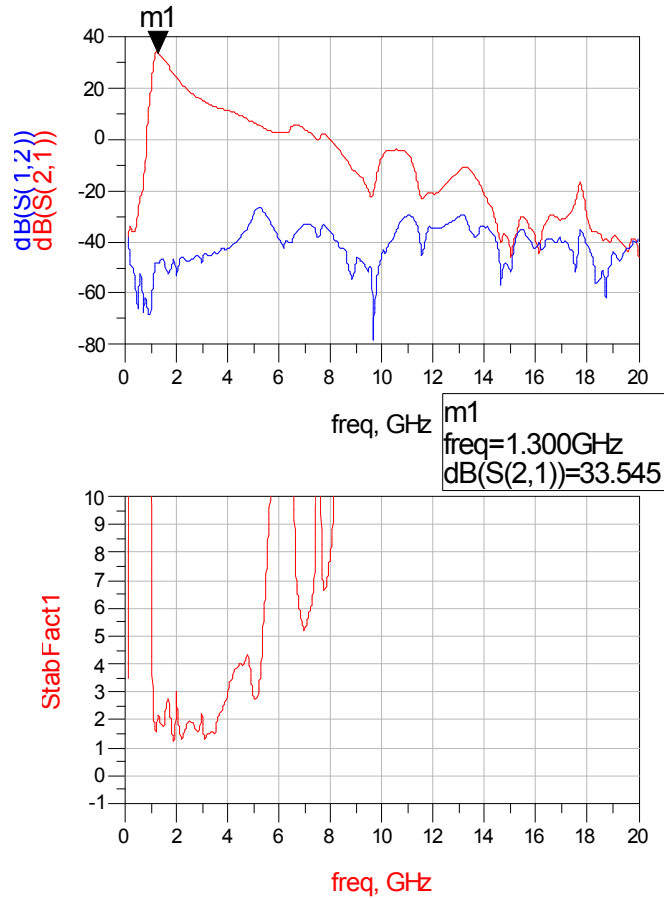
# 2 Stage ATF-36077 & MGA-61563 in Enclosure with Metal Divider Spanning Length of Box



Metal divider breaks up waveguide moding effect of box
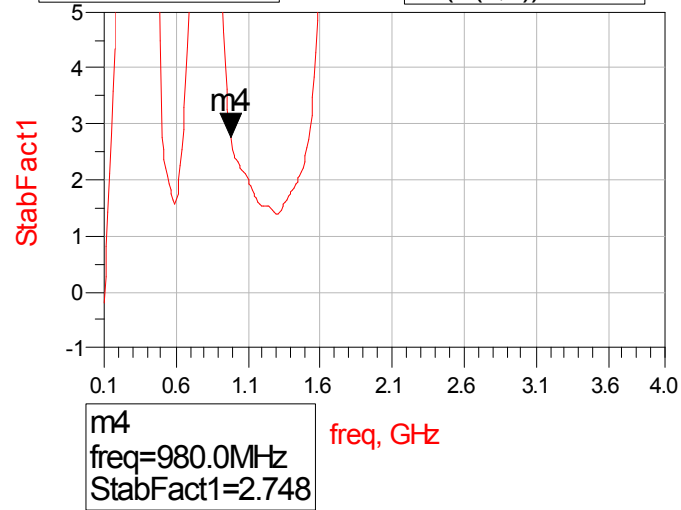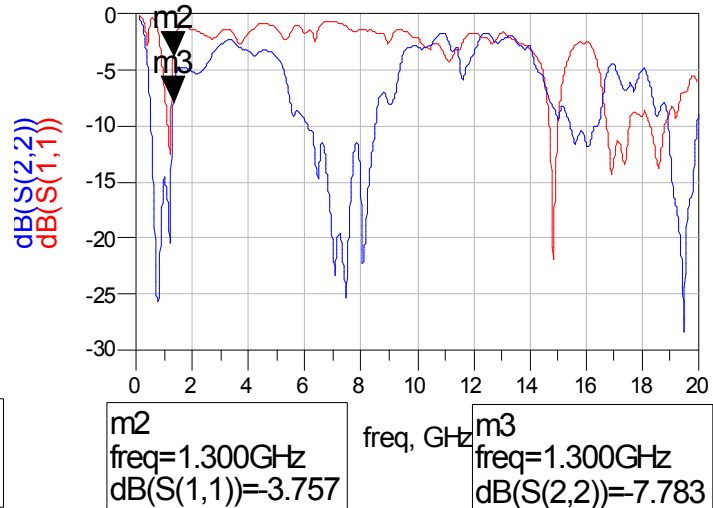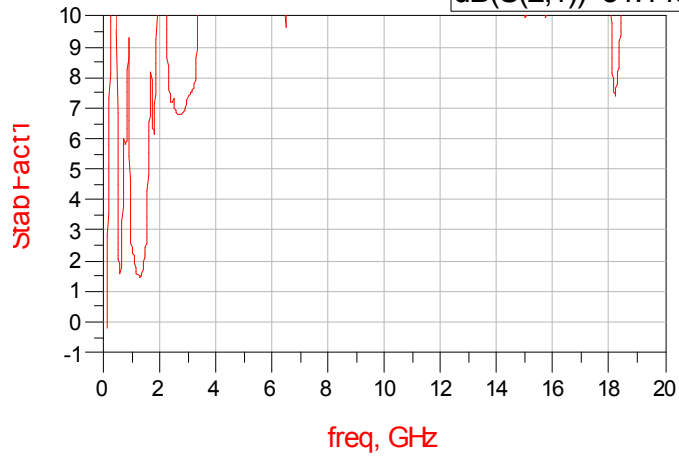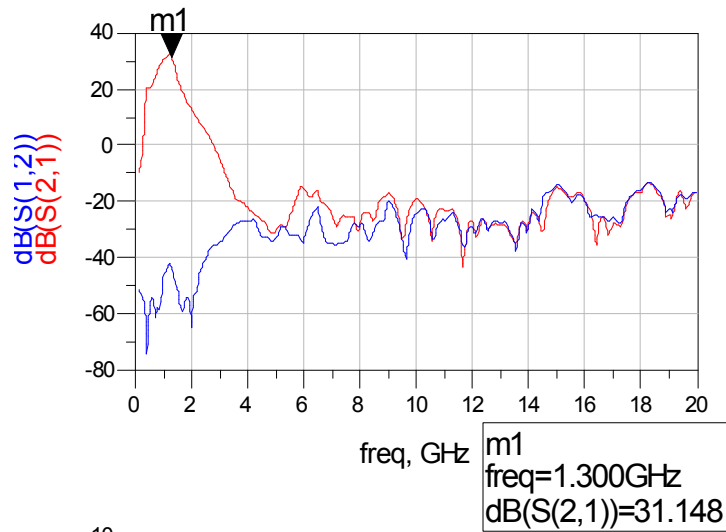
# Original 2 Stage LNA with ATF-36077 and ATF-21186



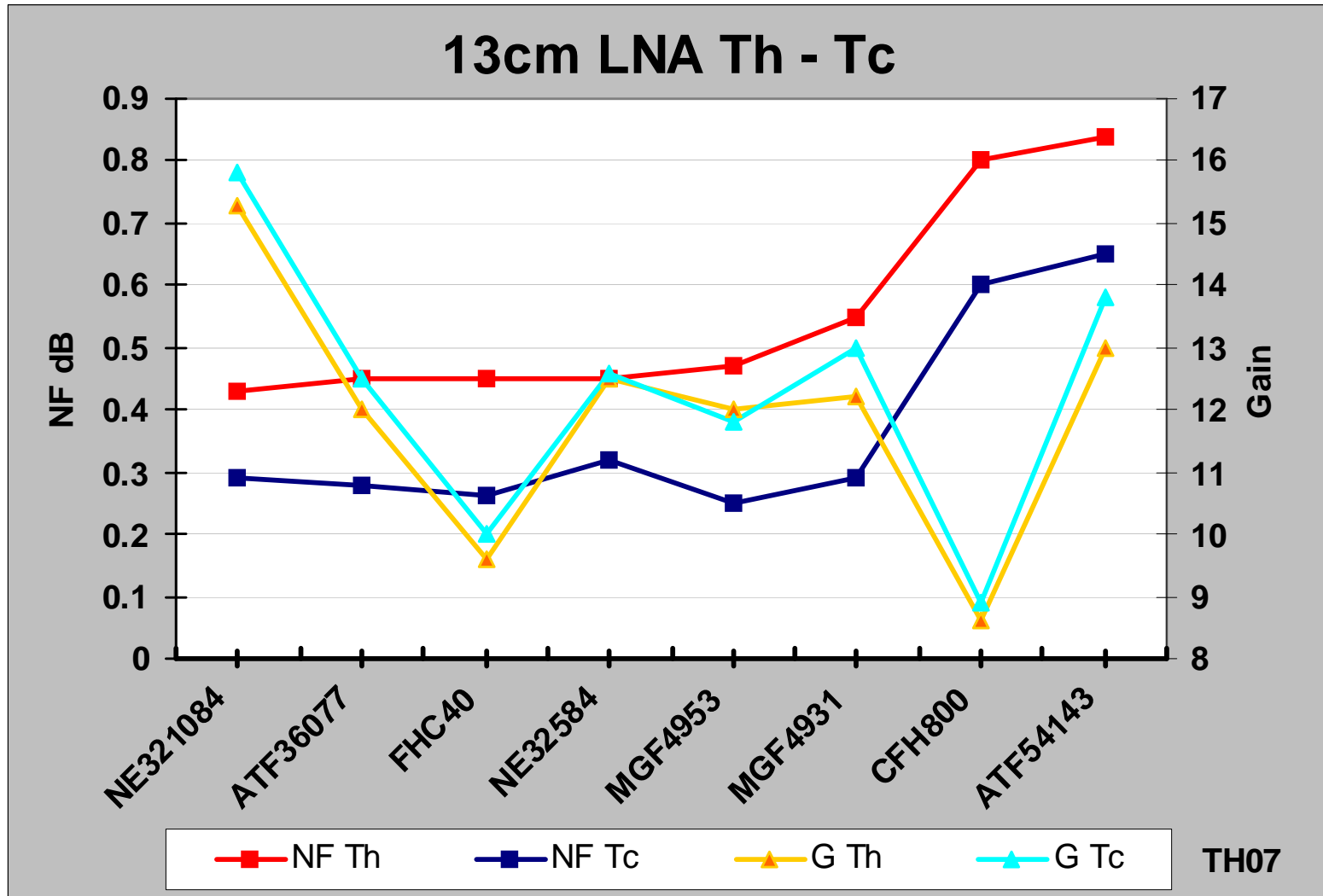

## Summary

**The MGA-61563 provided the additional gain desired while providing a lower noise higher IP3 second stage**

**LNA noise figures of 0.3 dB and 37 dB of associated gain have been demonstrated**

**Although the ATF-36077 / MGA-61563 cascade has been shown to provide K greater than 1, the increased gain is providing new challenges in enclosure design.**

**Any Questions?**